



Date: 17.05.2022

Roll No: 20951A04914 Name: Mohammed Sahail

Exp No: 05 Experiment Name: RC phase shift Oscillator

DAY TO DAY EVALUATION:

	Preparation	Algorithm	Source Code	Program Execution	Viva	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

[Signature]
Signature of Lab I/C

START WRITING FROM HERE:

Aim: To determine practical frequency of RC phase shift oscillator.
To draw frequency response compare it with theoretical frequency.

Determine maximum gain and bandwidth using bode plotter

Equipment needed:Hardware Requirements:

1. Analog Discovery
2. Instrument
3. Personal computer
4. Trainer Kit
5. connecting wires

Software Requirements:

1. Multisim software 14.0 edition
2. Waveform generator software

Background :-


RC shift oscillator has a CE amplifier followed by three sections of RC phase shift feedback networks. The output of the last stage is returned to the input of the amplifier. The values of R and C are chosen such that the phase shift of each RC section is 60° . Thus, the RC ladder network produces a total phase shift of 180° between its input and output voltage for the given frequency since CE amplifier produces 180° phase shift. The total phase shift from the base of the transistor around the circuit and back to the transistor will be exactly 360° or 0° . Thus frequency of oscillation is given by

$$F = 1/2RC6$$

* procedure *

1. Connect the circuit as shown in figure.
2. connect the 0.0022 F capacitors in the circuit and observe the waveform.
3. save the circuit and simulate
4. Calculate the time period and frequency of the resultant waveform. Compare the values with the practical circuit values.
5. Repeat the same procedure for $C = 0.033 \text{ F}$ and 0.01 F and calculate the frequency and tabulate as shown.
6. Find theoretical frequency from the formula $F = 1/2RC6$ and compare theoretical and practical frequency.

* Expected waveform *

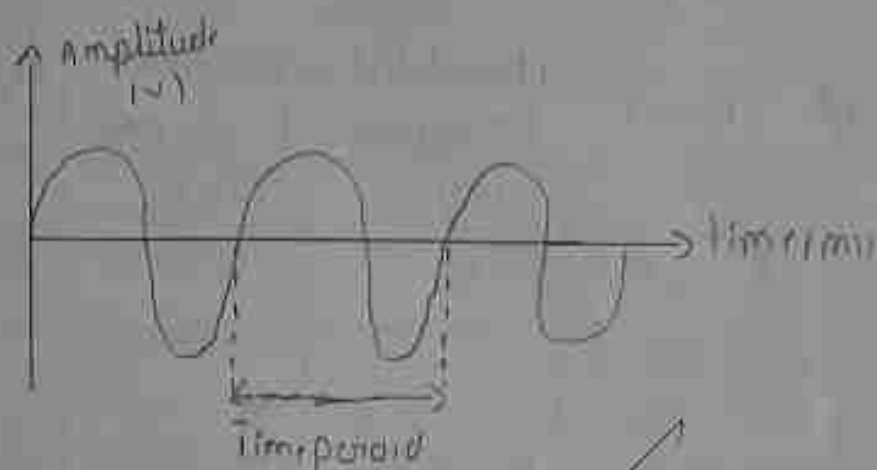

* Calculations *

* When $C = 0.003 \mu F$

$$f = \frac{1}{T} = 241.56$$

$$V_{p-p} = 8.83V$$

$$T = 2.47 \times 10^{-4} s$$

* When $C = 0.033 \mu F$

$$f = \frac{1}{T} = 1634.42$$

$$V_{p-p} = 8.4$$

$$T = 6.06 \times 10^{-4} s$$

* When $C = 0.01 \mu F$

$$f = \frac{1}{T} = 650.07$$

$$V_{p-p} = 8.871$$

$$T = 8.83 \times 10^{-3} s$$

* Result *




Design of RC phase shift oscillator has been performed & verified theoretical & practical values

\Rightarrow For $C = 0.0033 \mu F$ & $R = 10k\Omega$

Theoretical frequency = 241.56

practical frequency = 8.83

exp ✓

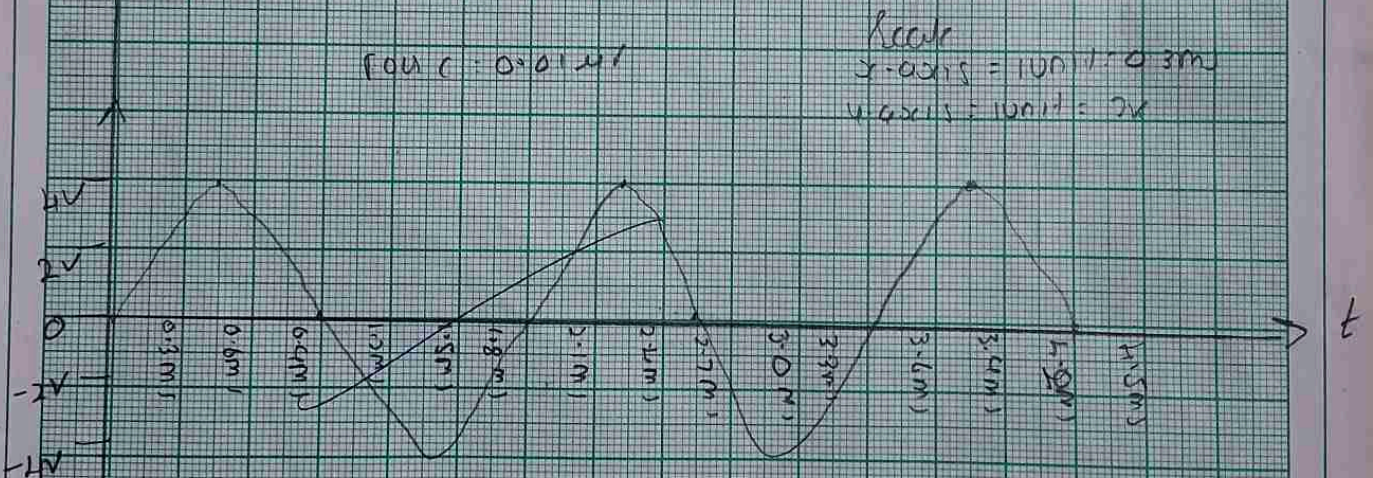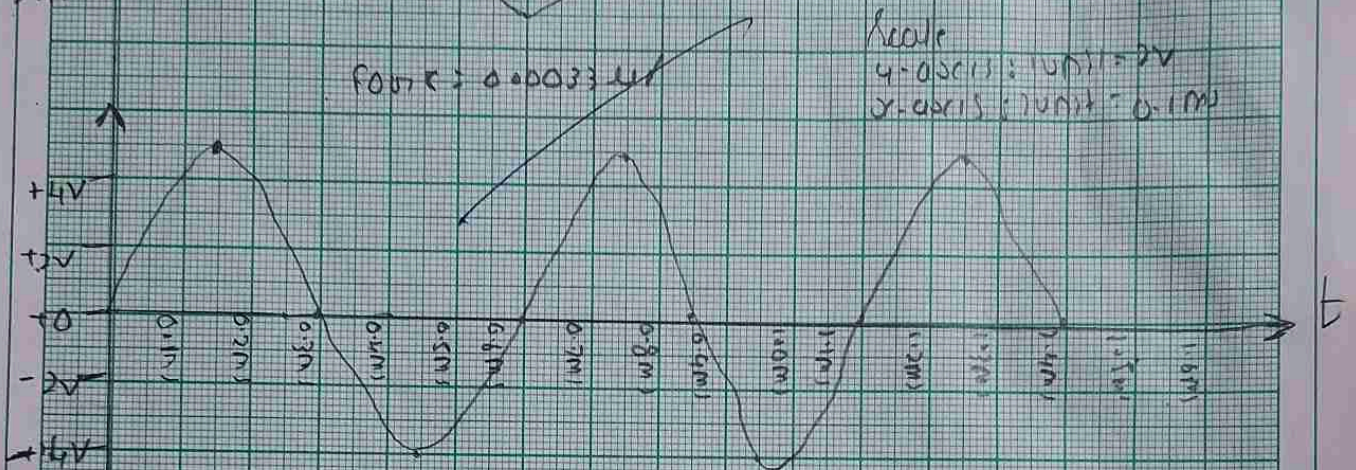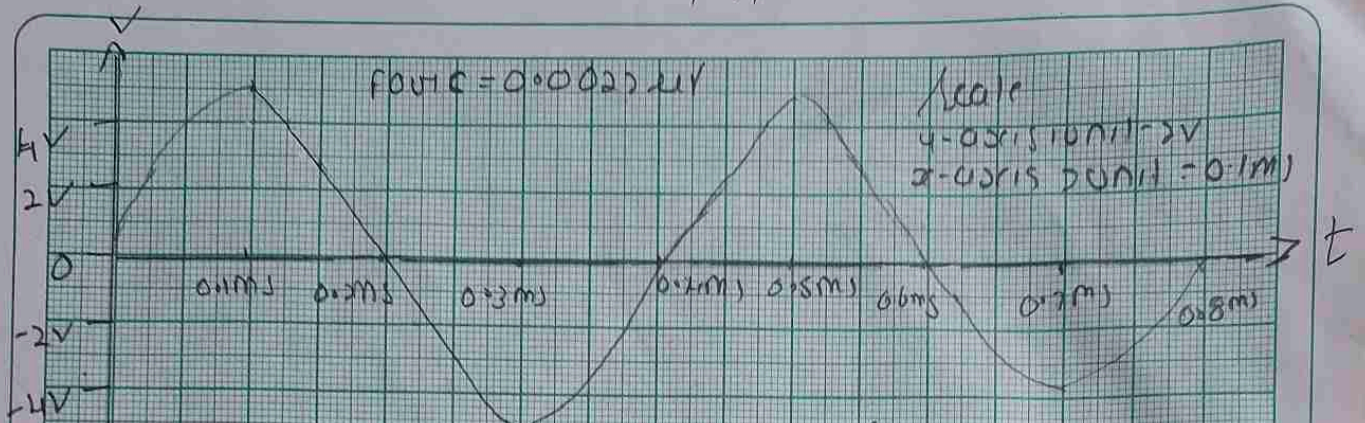

eg