



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Dundigal, Hyderabad - 500 043

LABORATORY WORK SHEET

Date: 14.06.22

Roll No: 20451A0494 Name: Mohammed Sahai

Exp No: 12 Experiment Name: Transistor switch

DAY TO DAY EVALUATION:

	Preparation	Algorithm	Source Code	Program Execution	Viva	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	3	4	19

Signature of Lab I/C

START WRITING FROM HERE:

Aim:- To study & observe switching characteristics of a transistor.

Apparatus:-

Resistor $\rightarrow 2.2k\Omega, 68k\Omega$ (1)


Transistor $\rightarrow BC107$ (1)

Bread board (1)


Analog discovery kit (1)

connecting wires

circuit Diagram

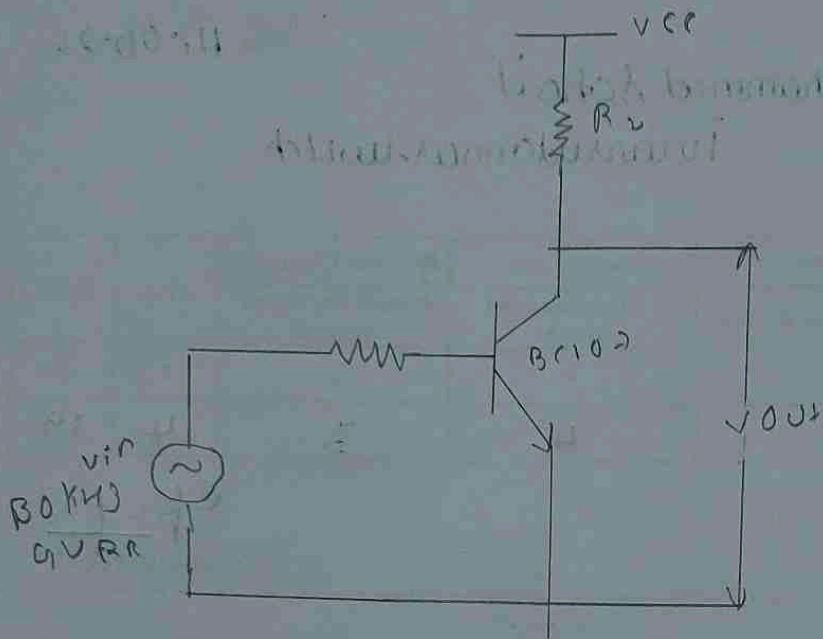

Expected waveform

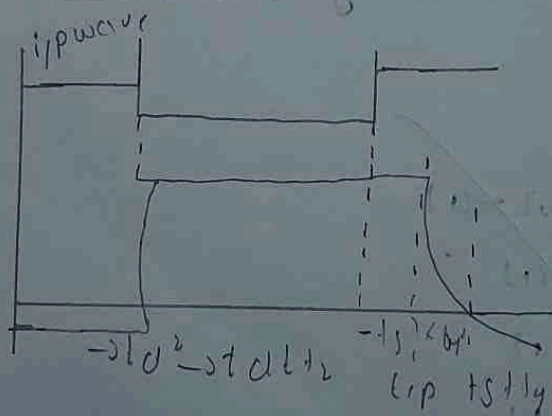

Procedure:-

- connect circuit switch on power supply & observe o/p of function generator on CRO.
- Adjust i/p signal amplitude such that o/p signal peaks to peak value is less than saturation level.
- Observe o/p waveform on CRO & note down the readings.
- Plot graph b/w i/p & o/p waveform at given input frequency.

calculations:-

- (1) $t_d = 0.2 \mu s$ (delay time) (2) $t_r = 1.5 \text{ ns}$ (rise time)
(3) $t_s = 400 \text{ ns}$ (settling time) (4) $t_f = 400 \text{ ns}$ (falling time)
 $V_{p-p} = 12.7 \text{ V}$

Result:- calculated t_d, t_r, t_f, t_s values & observed wave o/p and practical graph.

Voltage (V)

impulse

5V

0

0.5 1 1.5 2 2.5 3 3.5 4 4.5 5 5.5 6 6.5 (ms)

t_{on}

t_{off}

t_{on}

t_{off}

20