



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)  
Dundigal, Hyderabad - 500 043

## LABORATORY WORK SHEET

Date: 29.03.2022

Roll No: 20951A0494 Name: Mohammed Ismail

Exp No: 004 Experiment Name: Feedback Amplifiers

### DAY TO DAY EVALUATION:

	Preparation	Algorithm	Source Code	Program Execution	Viva	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Signature of Lab IC

### START WRITING FROM HERE:

Aim:- Concepts of Feedback and need for feedback in amplifiers.

1. Measure current shunt feedback amplifier circuit with and without capacitor.
2. Voltage series feedback amplifiers.
3. Determine frequency response for Voltage series with and without feedback amplifiers.
4. Draw frequency responses current shunt with and without capacitor is plotted.
5. Determine maximum gain and bandwidth using bode plotter.

Equipment needed:-

Hardware Requirements

1. Analog Discovery
2. Instrument



2. personal computer

3. Trainer Kit

4. Connecting jumper and connecting wires

### Software Requirements:-

1. Multisim software 14.0 edition.

2. Newform generator software


### Theory:-

Feedback plays a very important role in electronic circuit and the basic parameters, such as input impedance, output impedance, current and voltage gain and bandwidth, may be altered considerably by the use of feedback for a given amplifier. A portion of the output signal is taken from the output of the amplifier and is combined with the normal input signal and thereby the feedback is accomplished.

1. positive feedback

2. Negative feedback helps to increase the bandwidth, decrease gain, distortion, and noise, modify input and output impedance as desired. A current shunt feedback amplifier circuit is called a series-shunt feedback. The shunt connection at the input reduces the input impedance and the series connection at the output increases the output impedance.

## circuit diagram :-

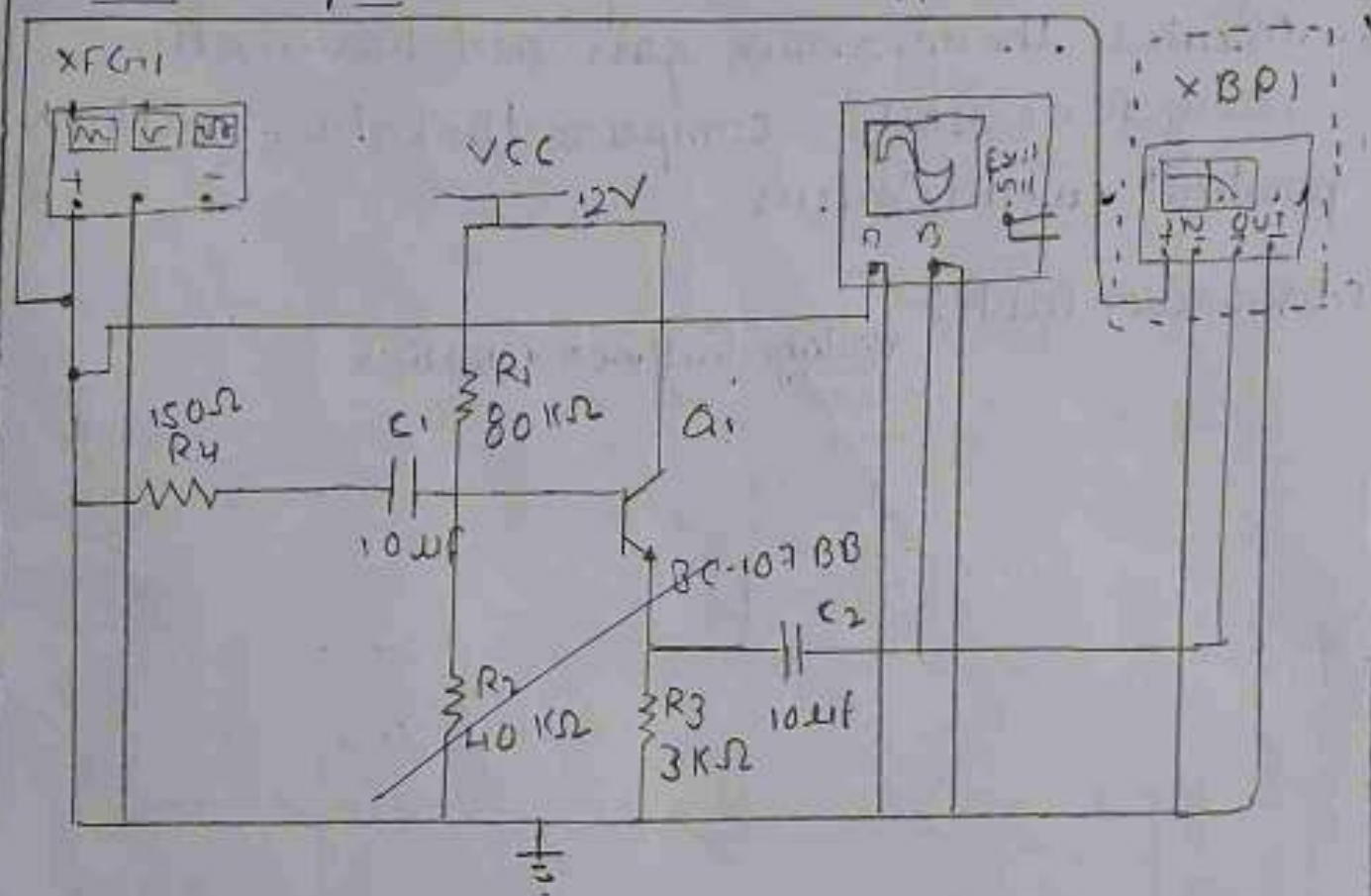

## Procedure

1. connect the circuit as shown in figure.
2. Adjust input signal amplitude in the function generator and observe an amplified voltage at the output without distortion.
3. By keeping input signal voltage, say at 50mV, Vary the input signal frequency from 0-1 MHz as shown in tabular column and note the corresponding output voltage.
4. Save the circuit and simulate.
5. For current shunt feedback amplifier with shunt capacitive voltage series feedback amplifier.



Repeat the above procedure

6. Calculate the maximum gain and bandwidth using Bode plotter. Compare the values with the practical circuit values.

Observation Table:-

voltage feedback amplifier

Frequency in Hz	Gain in DB
10K	-51.898
50K	-37.914
100K	-21.401
500K	-17.993
1M	-12.189
4M	-3.046
8M	-1.183
12M	-0.719
18M	-0.542
30M	-0.454
50M	-0.337
100M	-0.315

Current  
Voltage Feedback amplifier

Frequency	Gain	
	without capacitor	with capacitor
10Hz	-27.037	-23.745
20Hz	-21.064	-13.293
40Hz	-13.067	-2.548
60Hz	-11.839	4.22
100Hz	-7.074	13.248
200Hz	-4.17	25.174
400Hz	-4.1406	36.134
600Hz	7.245	40.484
800Hz	9.132	42.156
1KHz	10.326	42.785

2 kHz	12.564	43.3
3 kHz	13.141	43.341
5 kHz	13.472	43.367
10 kHz	13.631	43.373
40 kHz	13.677	43.348
100 kHz	13.674	43.144
400 kHz	13.679	41.101
800 kHz	13.643	37.632
1 MHz	13.621	36.078
3 MHz	13.151	27.413
6 MHz	12.382	22.414

### Calculations

→ Voltage series feedback

$$\text{Gain } A_{\text{max}} = 40.337$$

$$\begin{aligned} -3\text{dB gain} &= 40.337 - 3\text{dB} \\ &= 37.337\text{dB} \end{aligned}$$

→ Forward current shunt without capacitor

$$\text{Gain } |A|_{\text{max}} = 13\text{dB}$$

$$\begin{aligned} -3\text{dB gain} &= 13 - 3\text{dB} \\ &= 10\text{dB} \end{aligned}$$

→ Forward current shunt with capacitor


$$\text{Gain } |A|_{\text{max}} = 43\text{dB}$$

$$-3\text{dB gain} = 43 - 3\text{dB} = 40\text{dB}$$

Result: - plotted graph the frequency response of feedback amplifier

Fig.




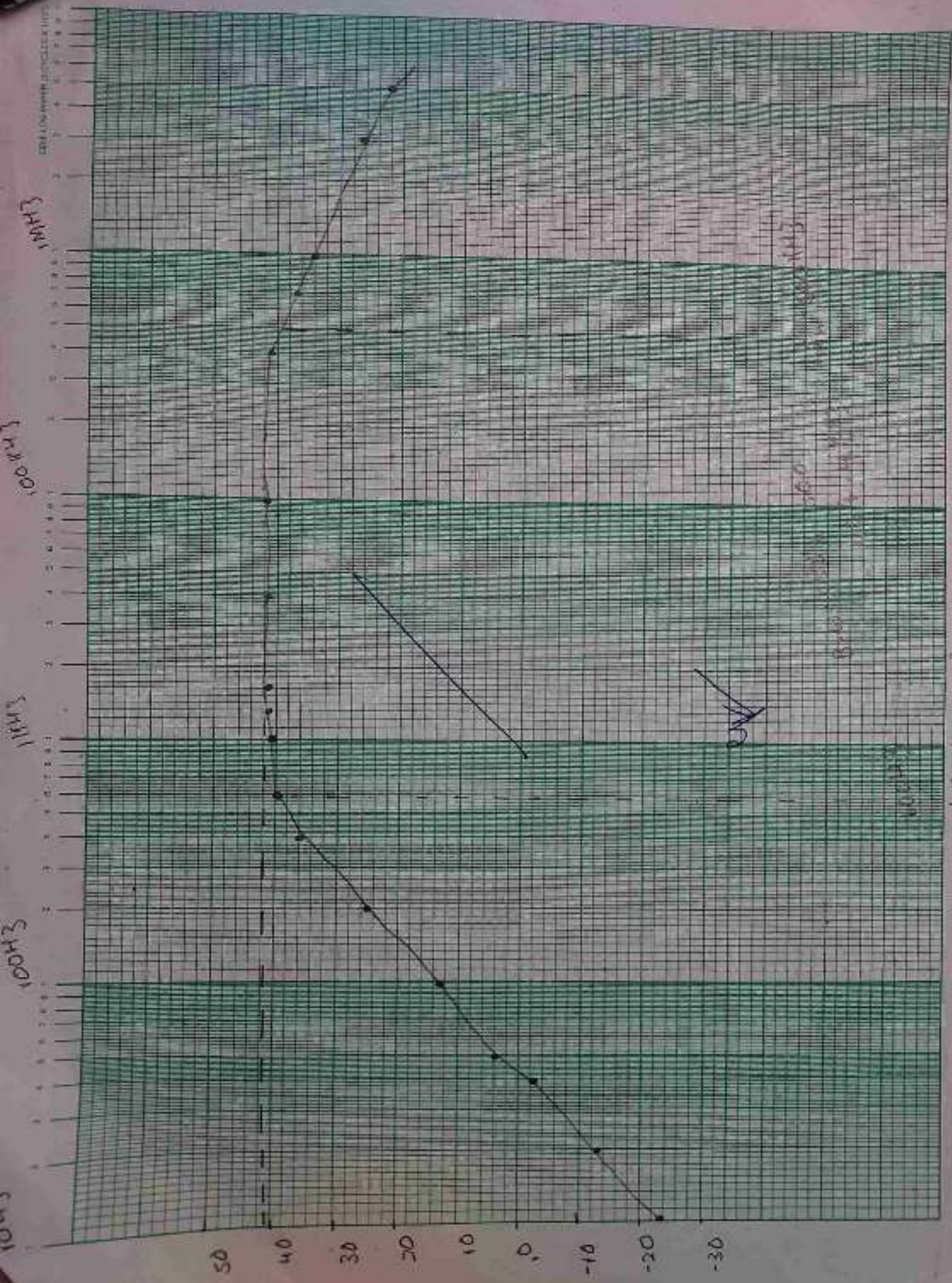


Current feedback Amplifier (with capacitor)



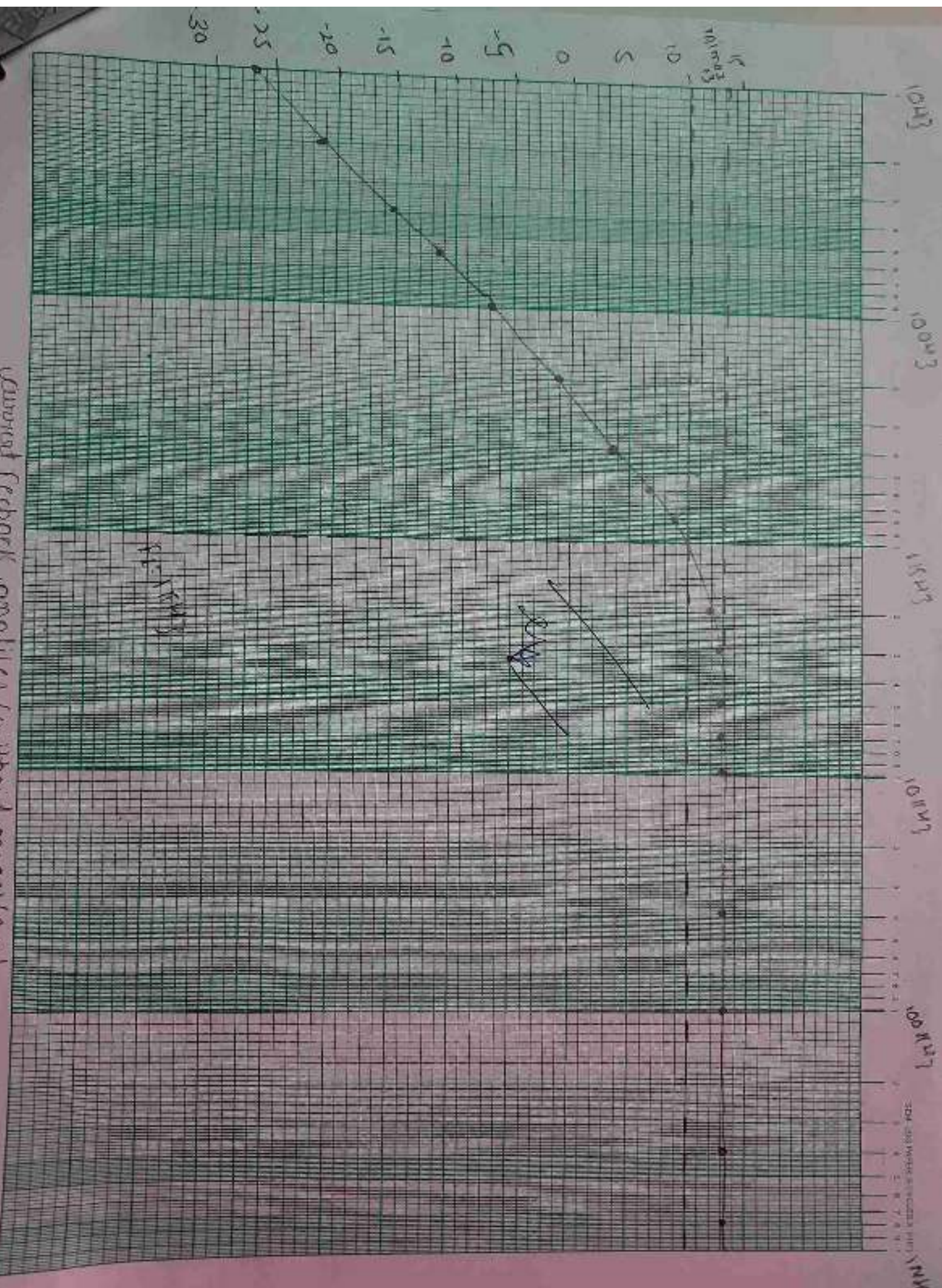Current feedback amplifier (with and without feedback)





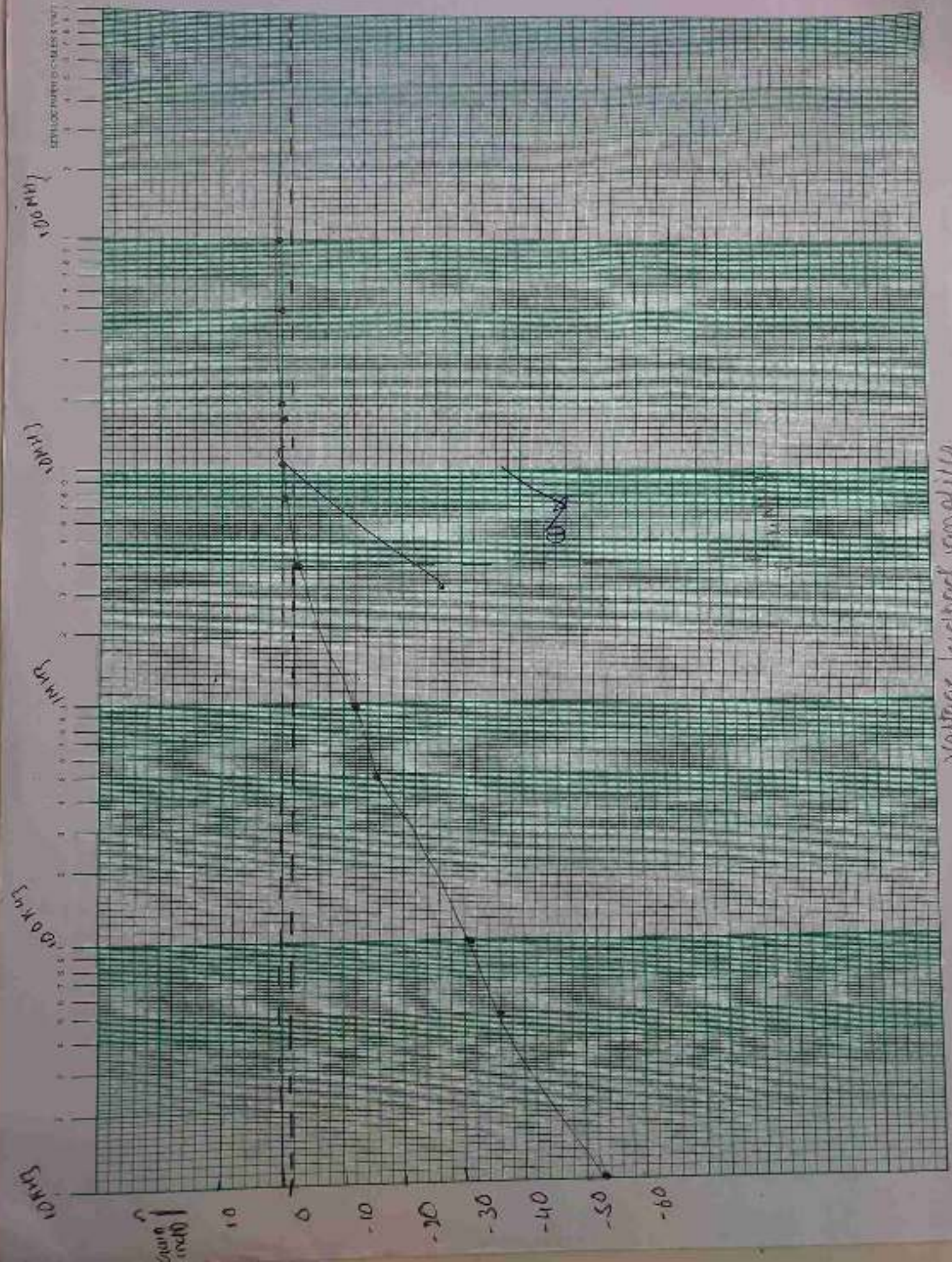

Voltage feedback amplifier