



Date: 03/06/2022

Roll No: 209S1A049, Name: Mohammed Saleh

Exp No: 07 Experiment Name: class A and class B power amplifiers

## DAY TO DAY EVALUATION:

	Preparation	Algorithm	Source Code	Program Execution	Viva	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	3	3	4	4	4	18

Signature of Lab UC

## START WRITING FROM HERE:


Aim:- To study and plot the frequency response of class A and class B power amplifiers.

Software Required:- Multisim analog circuit edition 13.0


components required:-

- Trainer kit
- Transistors
- Resistors
- capacitors
- DC supply
- Ammeter
- Voltmeter
- Function generator
- CRO
- connecting wires and probes.

\*circuit diagram\*

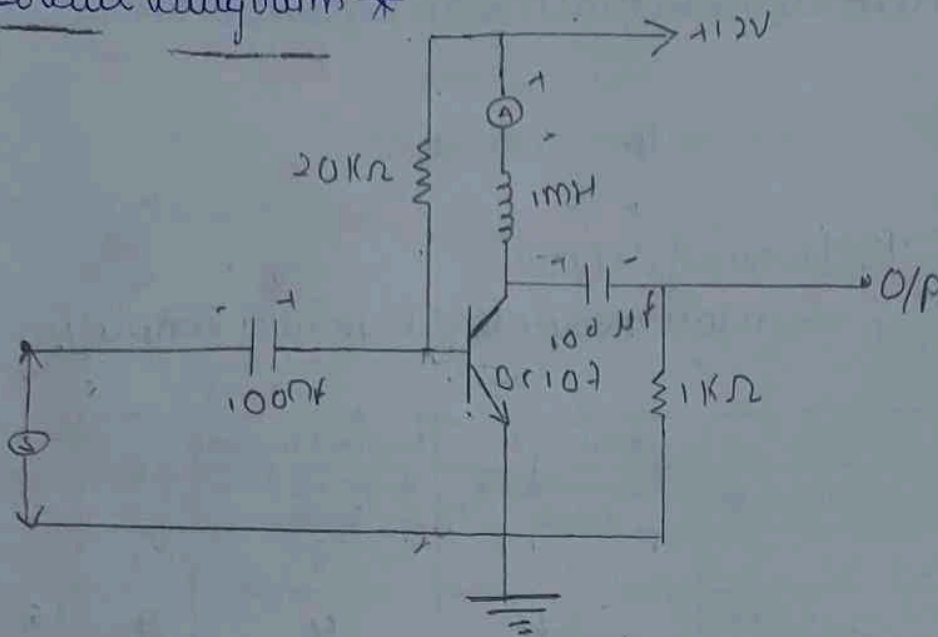

class A power amplifier

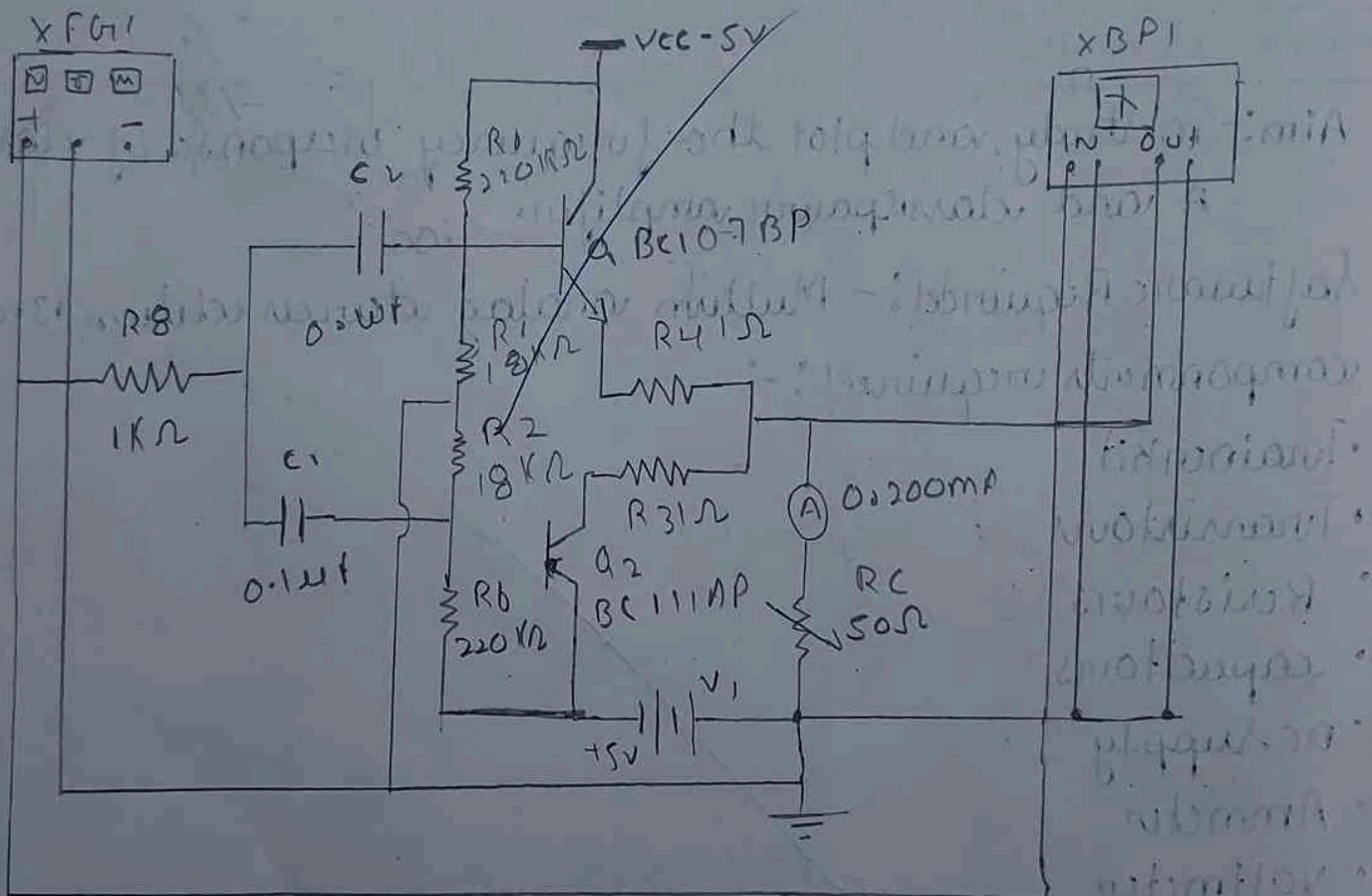

class B - power amplifier




### \* Theory \*

power amplifiers are mainly used to deliver more power to deliver more power to the load. To deliver more power it requires large input signals so generally power amplifiers are provided by a series of voltage amplifiers. In class A Q-point is located in the middle of the load line. Under zero signal condition, maximum power dissipation occurs in the transistors. The max theoretical efficiency is 50%.

### Procedure:-

- connect the circuit as shown in the figure.
- Adjust input signal amplitude in the Function generator and observe an amplified voltage at the O/p without distortion.
- By keeping input signal voltage say at 150 mV, vary the input signal frequency from 0-1 MHz as shown in tabular column and note the corresponding O/p voltage.
- Measure & note the zero signal DC current by disconnecting the function generator from the circuit.
- Calculate efficiency & plot the graph.

### \* Expected graph \*

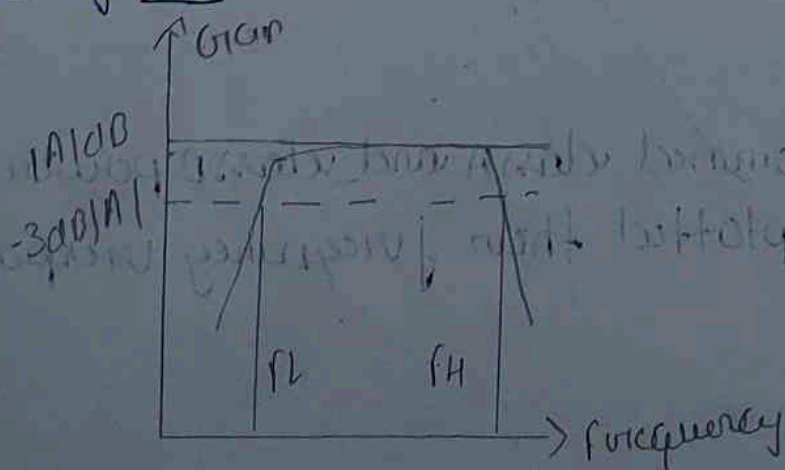

## \* Tabular column \*

Frequency	Gain of class-A	Gain of class-B
50Hz	12.7dB	-15.4dB
100Hz	18.8	-9.5
200Hz	24.8	-3.7
500Hz	33.2	3.6
1KHz	36.8	8.4
5K	40.8	12.4
7K	44.1	13.13
10K	44.2	13.2
30K	44.4	13.2
40K	44.4	13.2
100K	44.4	13.2
500K	44.4	13.6
800K	38.4	11.7
1M	37.4	

## \* calculations \*

$$\text{class A } BW + f_M = f_c$$

$$\text{class B } = BW + f_H - f_L$$

$$= 900 - 14K \text{ Hz}$$

$$= 898.6 \text{ KHz}$$


$$= 1M + 1.7K \text{ Hz}$$

## \* Result \*

Then performed class A and class B power amplifiers and plotted their frequency response.




# CLASS A - POWER AMPLIFIER

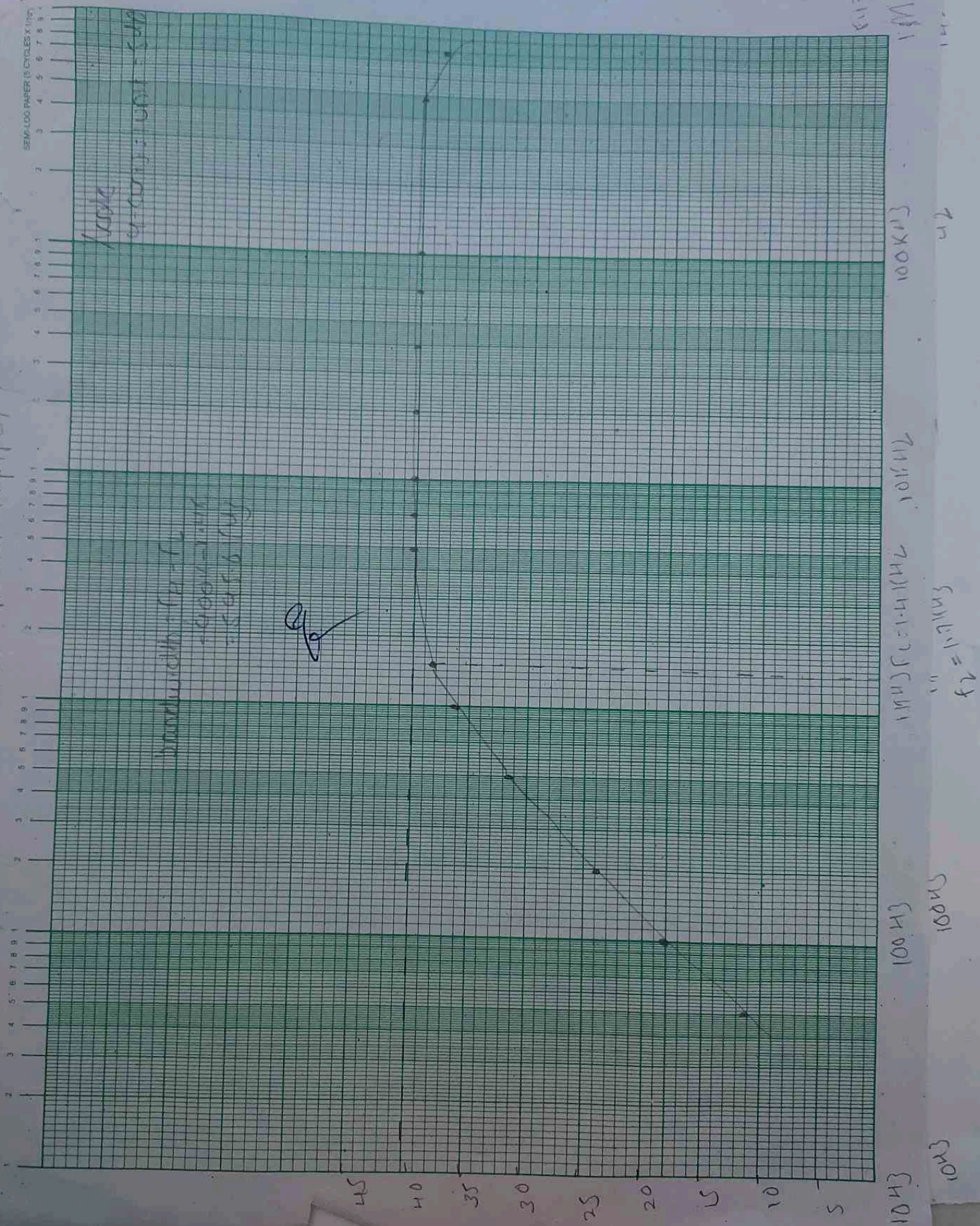



# class-B power amplifier

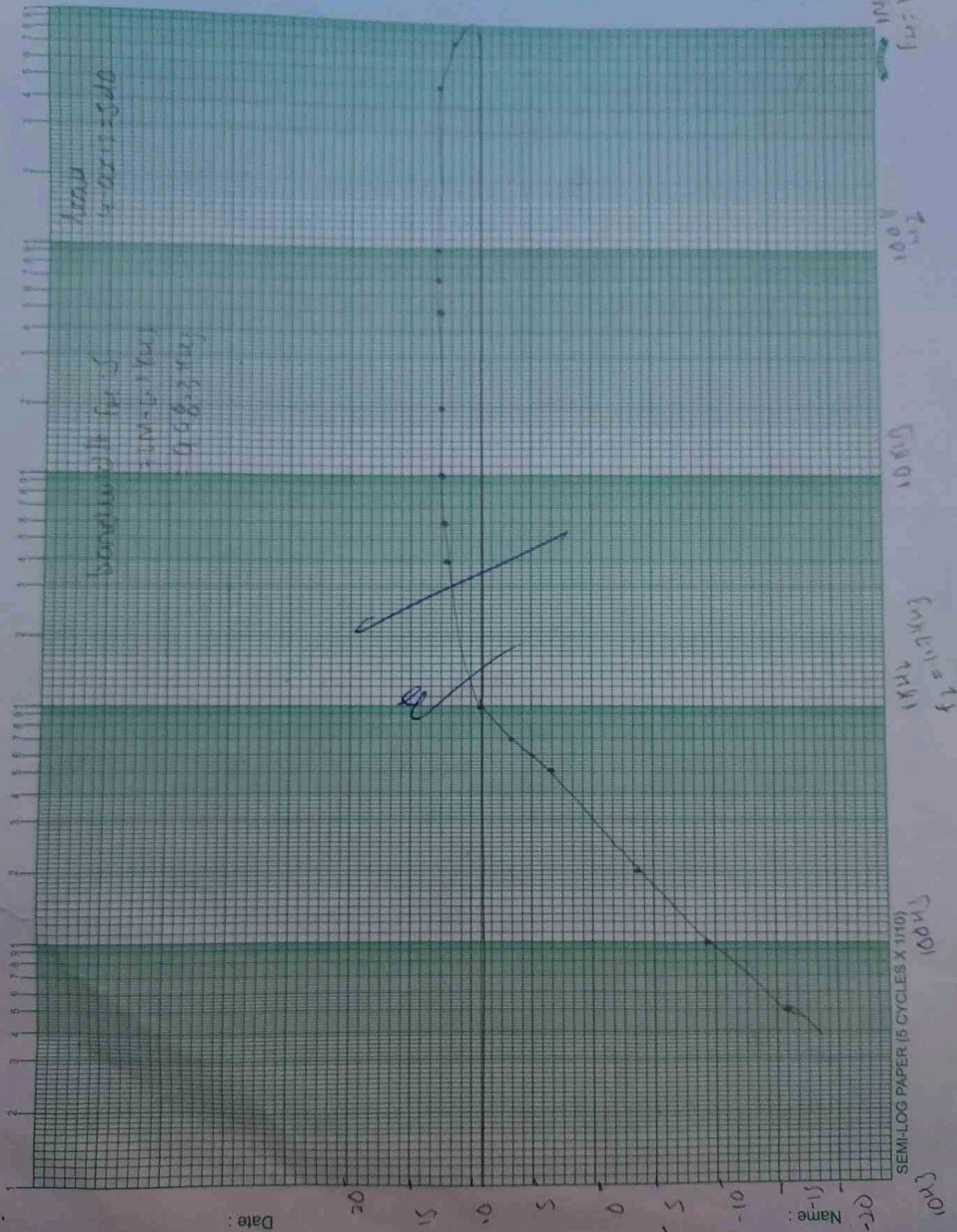

SEMI-LOG PAPER (5 CYCLES X 1/10)

Name: \_\_\_\_\_

Date: \_\_\_\_\_