



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)
Dundigal, Hyderabad - 500 043

LABORATORY WORK SHEET

Date: 09.06.2022

Roll No: 20951A0494 Name: Mohammed Asheer

Exp No: 08 Experiment Name: Linear wave shaping circuit

DAY TO DAY EVALUATION:

	Preparation	Algorithm	Source Code	Program Execution	Viva	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	3	3	3	4	4	17

Signature

Signature of Lab I/C

START WRITING FROM HERE:

Aim: To design low pass RC and high pass RC for different conditions & verify their response for a square wave i/p of given i/p frequency.

Equipment Needed:-

- Trainer kit
- personal computer
- connecting wires
- Resistors - $100k\Omega$
- Capacitors - $0.1\mu f$, $0.01\mu f$, $0.0001\mu f$


Software Required:-

- waveform generator software
- multisim software








Theory:-

High pass RC circuit:- The reactance of the capacitor depends upon the frequency of operation. At very high frequency the

circuit diagram

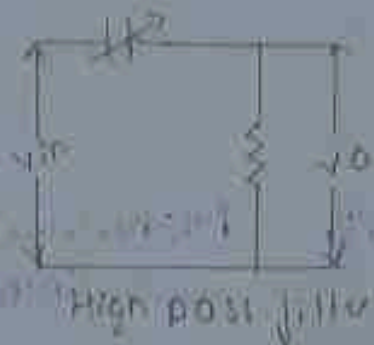

Expected waveform

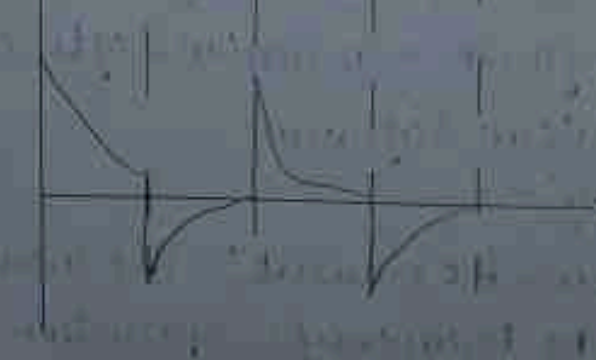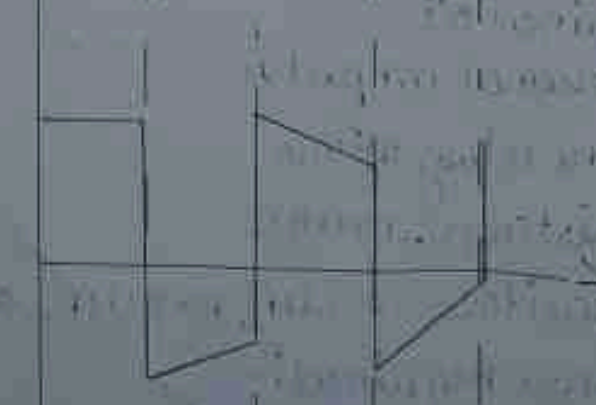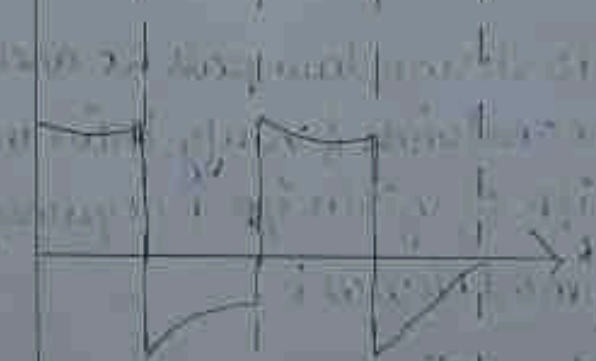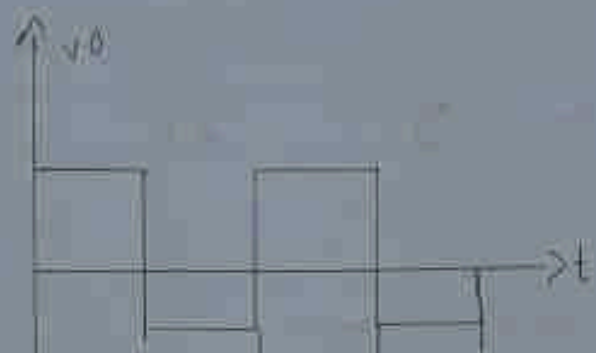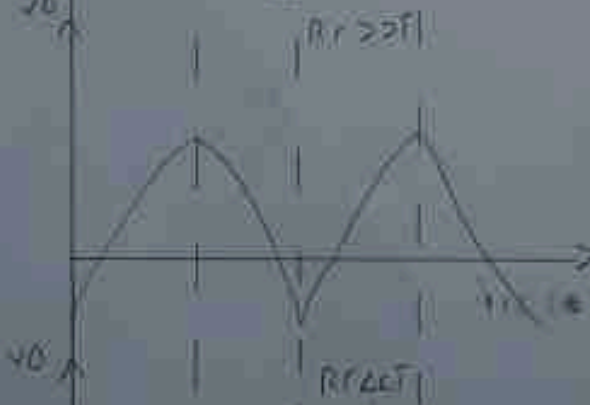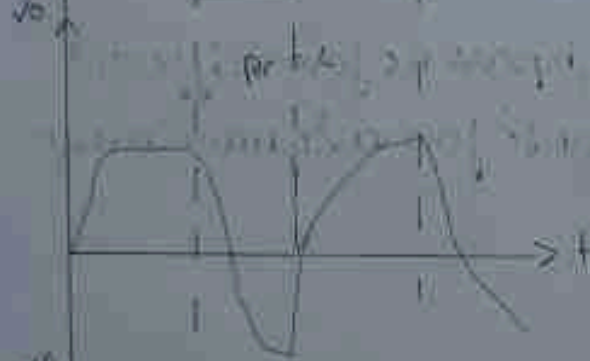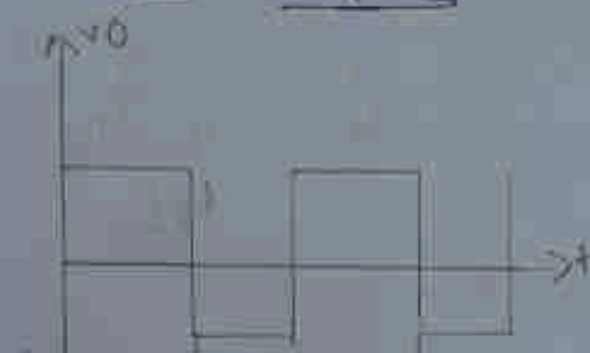

the reactance of the capacitor is Zero. Hence the capacitor acts as short circuit. As a result the entire input appears at the capacitor is infinite. So the capacitor acts as open circuit. Hence no input reaches the output. Since the circuit allows only high frequencies therefore it is called as high pass RC circuit.

Low pass RC circuit: The reactance of the capacitor depends upon the frequency of operations. At very high frequencies the reactance of the capacitor is 0. Hence the capacitor acts as s.c. As a result the o/p will fall to 0. At low frequencies the reactance of the capacitor is infinite. So the capacitor acts as o.c. As a result the entire i/p appears at the output since the circuit allows only low frequencies. Therefore it is called as low pass RC circuit.

* Procedure *

- connect the circuit as per circuit diagram.
- Apply the square wave input to the circuit $V_p = 10V_{p-p}$
 $f = 1kHz$
- Calculate the time constants of the circuit by connecting one of the capacitor provided.
- Observe the o/p waveform for different input frequencies as shown in tabular column for different time constants.

* Tabular column *

R	C	$\tau = RC$	Parallel time period	condition
100 k Ω	0.01 μ F	0.001 s	1 ms	$RC > 2T$
100 k Ω	0.01 μ F	0.001 s	1 ms	$RC = T$
100 k Ω	0.001 μ F	0.1 ms	1 ms	$RC < T$

R	C	$\tau = RC$	Parallel time period	condition
100 k Ω	0.1 μ F	0.01 s	1 ms	$RC > 2T$
100 k Ω	0.01 μ F	0.001 s	1 ms	$RC = T$
100 k Ω	0.001 μ F	0.1 ms	1 ms	$RC < T$

calculations:-

The critical time period:-

$$\tau = RC$$

$$(i) R = 100k, C = 0.01 \mu F$$

$$\tau = 100 \times 10^3 \times 0.01 \times 10^{-6}$$

$$= 0.001 s$$

$$(ii) R = 100k, C = 0.001 \mu F$$

$$\tau = 100 \times 10^3 \times 0.001 \times 10^{-6}$$

$$= 0.1 ms$$

$$(iii) R = 100k, C = 0.1 \mu F$$





$$\tau = 100 \times 10^3 \times 0.1 \times 10^{-6}$$


$$= 10 ms$$

* Result *

Hence, designed the low pass & high pass RC circuit and observed the output waveforms.


High Pass Filter RC Circuit

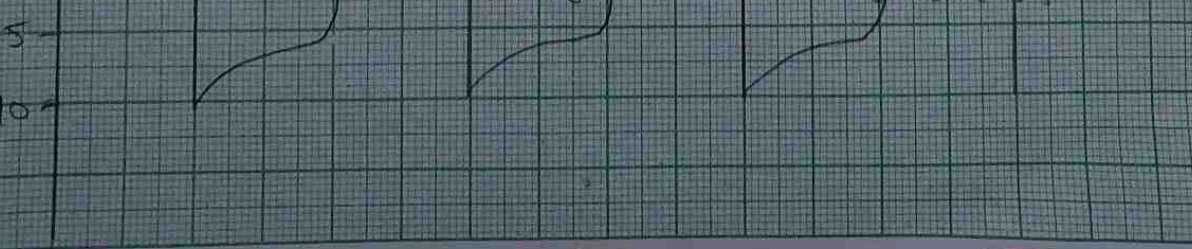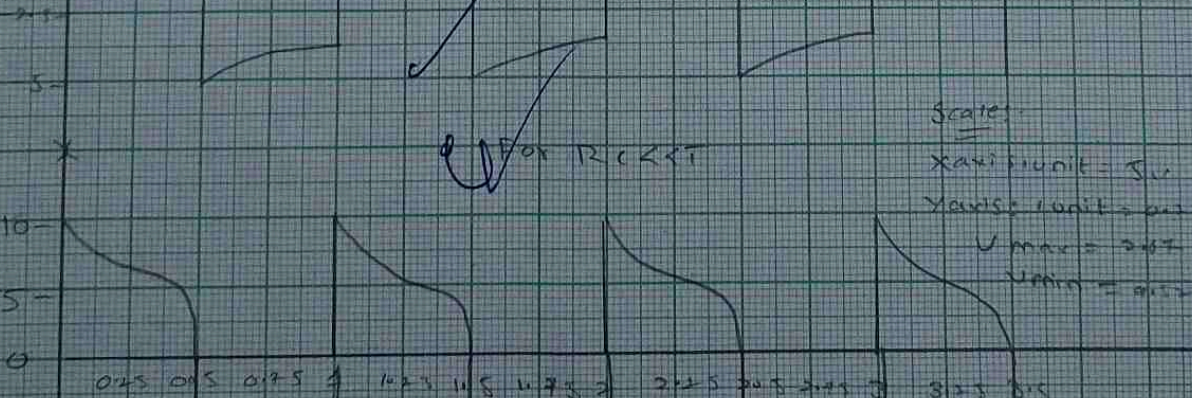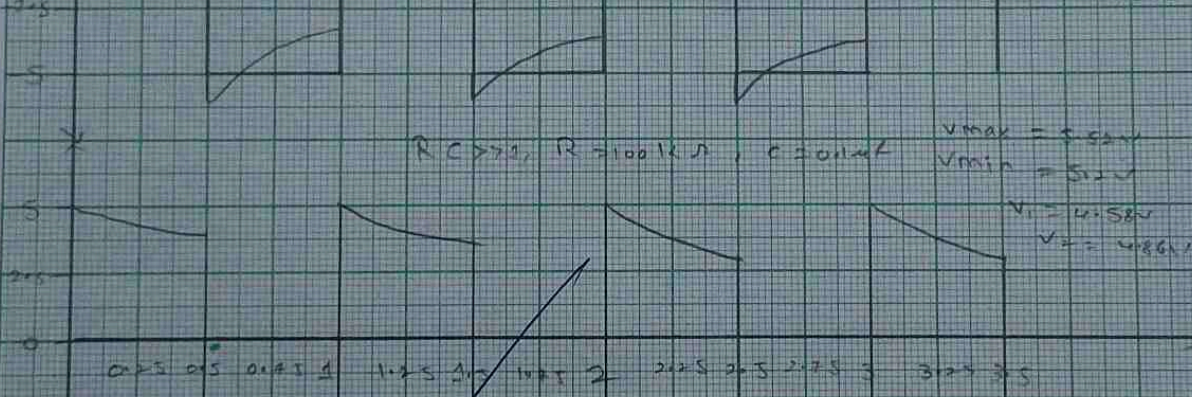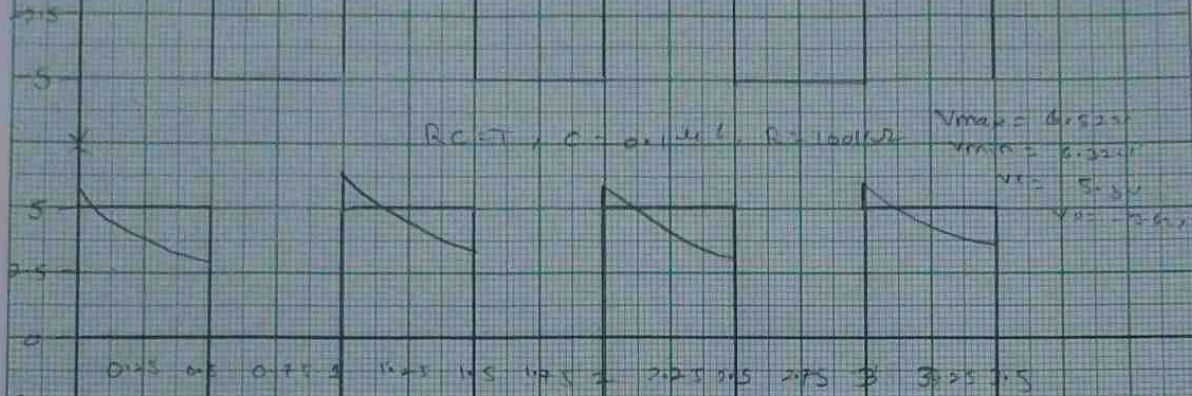

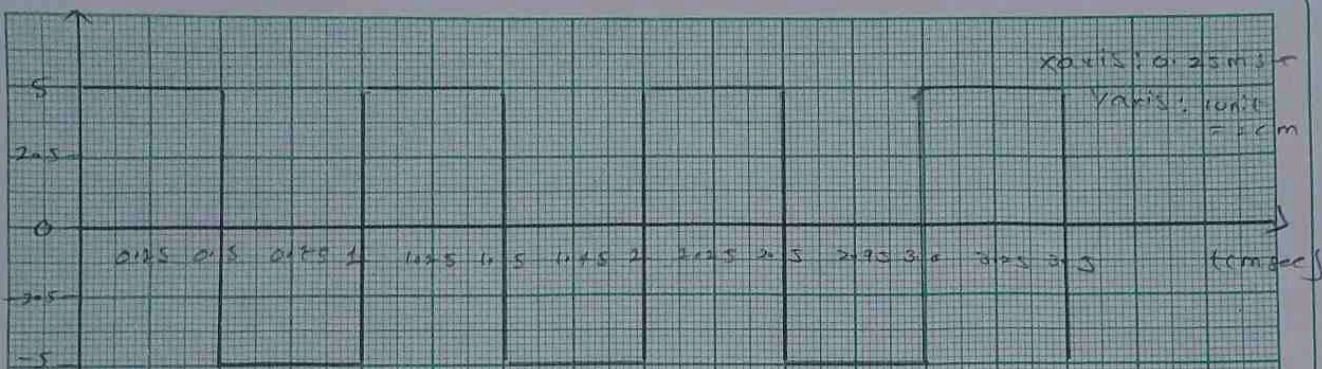


For $R_C = 1$, $R = 100k\Omega$, $C = 0.1\mu F$

$V_{max} = 1.3V$
 $V_{min} = 1.25V$

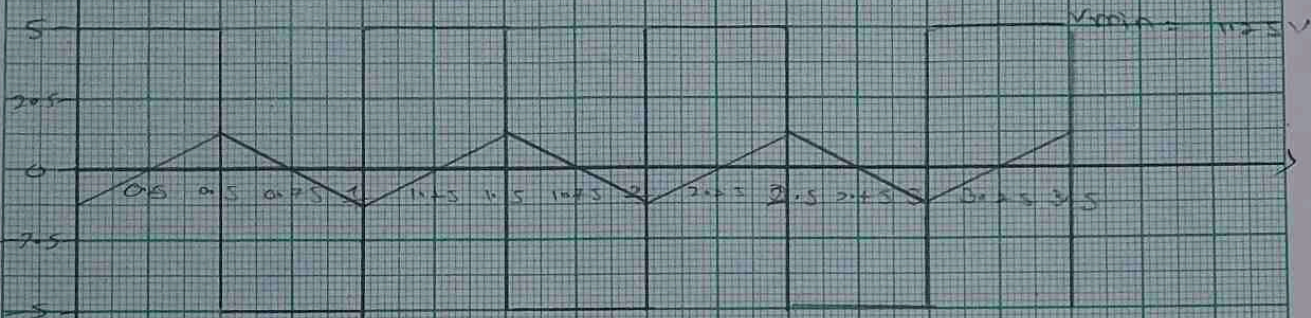

For $R_C < 1$, $R = 100k\Omega$, $C = 0.1\mu F$

$V_{max} = 4.55V$
 $V_{min} = 4.5V$

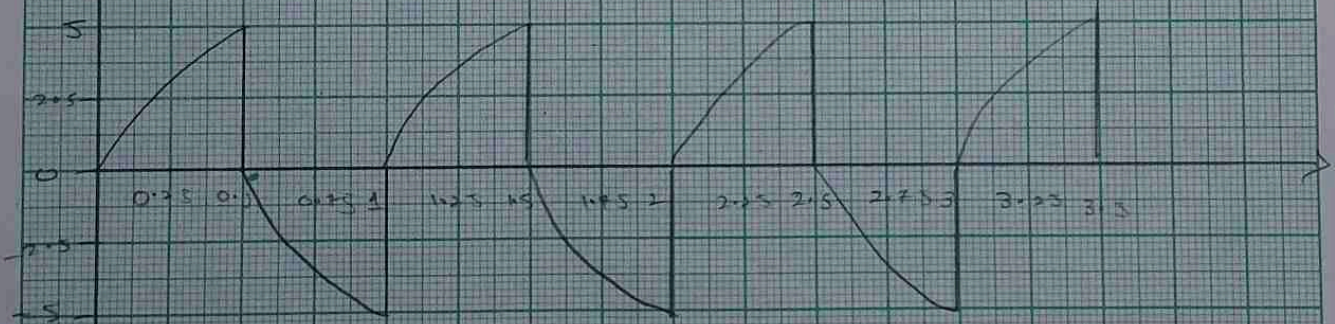

For $R_C \gg 1$, $R = 100k\Omega$, $C = 0.1\mu F$

X-axis: unit

Y-axis: unit
 $V_{max} = 1.86$
 $V_{min} = 1.84$

