



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)
Dundigal, Hyderabad - 500 043

LABORATORY WORK SHEET

Roll No. 20451A0494 Name: Mohammed Ishtaiq

Date: 22.3.2022

Exp No: 2 Experiment Name: Two Stage RC-coupled Amplifier

DAY TO DAY EVALUATION:

	Preparation	Algorithm	Source Code	Program Execution	Viva	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Signature of Lab I/C

START WRITING FROM HERE:

Aim:

1. To plot frequency response of RC coupled amplifier with a pair of tuned emitter capacitors of 10 μ F and 100 μ F
2. To calculate gain
3. To calculate bandwidth

Software Required

Multisim Analog Device Edition 13.0


Components and Equipments Required

1. Trainer Board containing
DC supply voltage \rightarrow 12V
NPN Transistor \rightarrow BC107 (1)


At low frequencies reactance of coupling capacitors (X_C) is quite high and hence very small part of signal will be pass through from one stage to next stage

At high frequencies reactance of inter electrode capacitance is very small and behaves as short circuit. This increases loading effect on next stage & service to reduce voltage gain due to these reasons voltage gain drops at high frequencies At

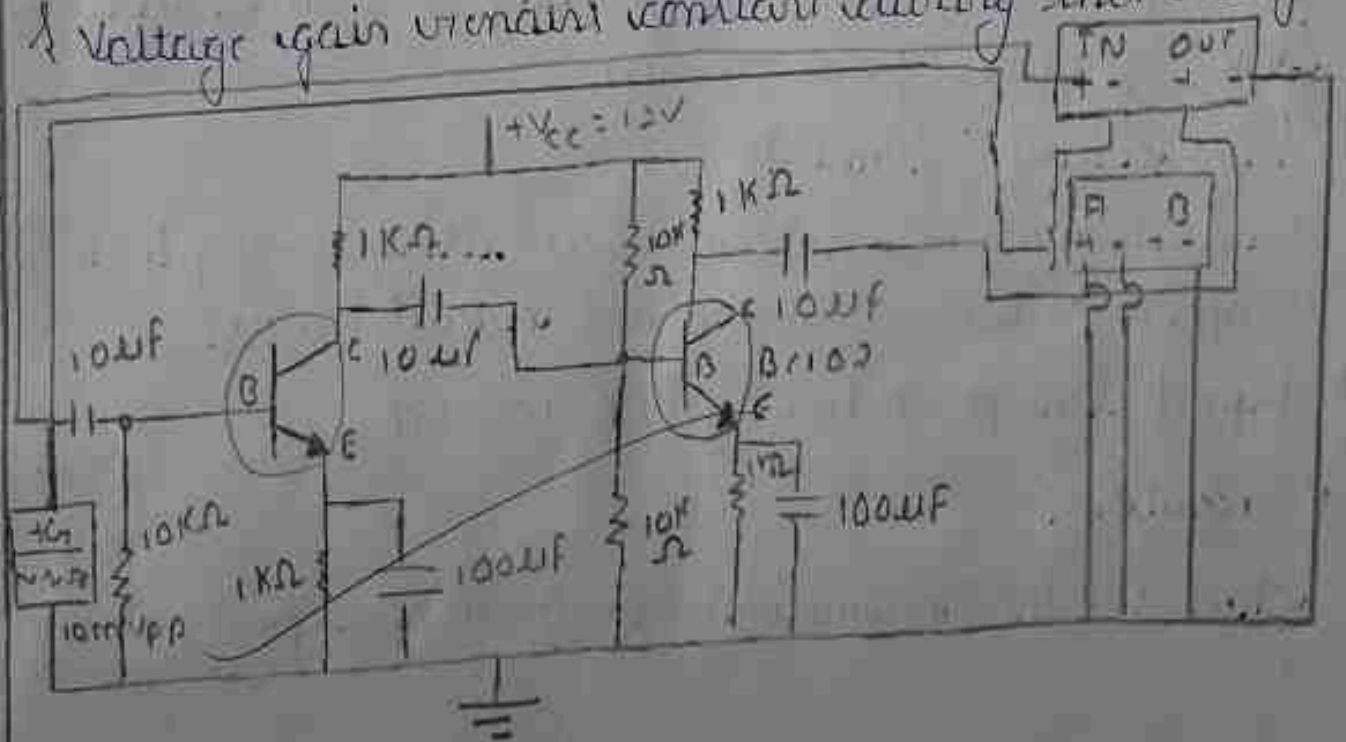mid frequencies effect of coupling capacitors is negligible and acts like short circuit, where as inter electrode capacitors acts like open circuit. So, circuit becomes resistive at mid frequencies & voltage gain remains constant during this range



Expected Graph:-

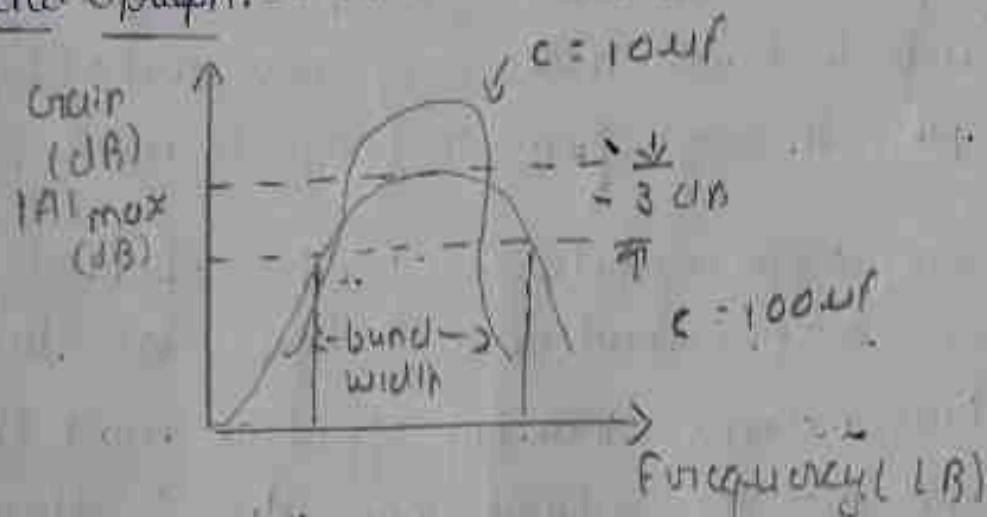

Procedure:-

1. Connect circuit as shown in fig for $10 \mu F$
2. Adjust I/P signal amplitude in function generator, & observe an amplified voltage at O/P without distortion.
3. By keeping I/P signal voltage, say at 50 mV , vary I/P signal frequency from $0-1 \text{ MHz}$
4. Save circuit & simulate
5. Calculate max gain & bandwidth using Bode plotter. Compare values with practical circuit values.
6. Repeat same procedure for $C = 100 \mu F$

Precautions:-

check whether connections are made properly or not

Tabular form:-

$$V_{in} = 10\text{mV} \quad \text{Gain}(A_v) = V_o / V_{in}$$

$$V_o = 2$$

S.No	C = 10 μ F		C = 100 μ F	
	Frequency (Hz)	Gain (dB) $20 \log(V_o/V_{in})$	Frequency (Hz)	Gain (dB) $20 \log(V_o/V_{in})$
	10 Hz	288.783 mV	28.8784	29.2116
	20 Hz	1.184 V	118.6	41.48
	30 Hz	2.662 V	375.9	48.50
	40 Hz	3.454 V	490	51.58
	50 Hz	4.9 V	543.3	53.80
	60 Hz	5.923 V	656.4	55.45
	70 Hz	6.564 V	720.5	56.34
	100 Hz	7.205 V	753.1	57.15
	200 Hz	7.521 V	76.9	57.52
	500 Hz	7.640 V	773.4	57.71
	1 KHz	7.734 V	774.4	57.77
	2 KHz	7.744 V	775.1	57.77
	5 KHz	7.751 V	774.4	57.78
	10 KHz	7.744 V	773.8	57.77
	50 KHz	7.738 V	784.0	57.88
	100 KHz	7.840 V	674.4	57.88
	500 KHz	6.744 V	674.8	56.58
	1 MHz	6.748 V	604.1	56.58
	50 KHz	1.041 V	1070.1	44.45
	70 KHz	1.671 V	117.4	41.39
	80 KHz	1.174 V	101.8	40.15
	100 KHz	744.67 mV	74.46	38.00
	100			

calculations

1. $f_{07} = 10 \mu F$

Gain =

$$\text{Bandwidth} = [f_H - f_L]$$

2. $f_{07} = 100 \mu F$

Gain =

$$\text{Bandwidth} = [f_H - f_L]$$

maximum gain dB = 57.88 dB

$$f_H = 100 \text{ kHz}$$

$$f_L = 70 \text{ Hz}$$

$$\text{Bandwidth} = f_H - f_L$$

$$= 100 \text{ kHz} - 70 \text{ Hz}$$

$$= 99.93 \text{ kHz}$$

To find the band width

$$= \text{Gain in dB} - 3 \text{ dB}$$

$$= 57.88 \text{ dB} - 3 \text{ dB}$$

$$= 54.88 \text{ dB}$$

Precautions:-

check whether the connections were made properly or not.

Result:-

Hence Frequency Response of RC coupled (2 stage) amplifier for $10 \mu F$ and $100 \mu F$ is plotted.

Semi-log paper (cycles x 1/10⁷)

