

APC



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)
Dundigal, Hyderabad - 500 043

LABORATORY WORK SHEET

Date: 4.06.2022

Roll No: 20451A0494 Name: Mohammed Sahail

Exp No: 06 Experiment Name: Hartley and Colpitts Oscillators

DAY TO DAY EVALUATION:

	Preparation	Algorithm	Source Code	Program Execution	Viva	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	3	3	3	3	16

Signature of Lab I/C

START WRITING FROM HERE:

Aim: - To find practical frequency of a Hartley and Colpitts oscillator and to compare it with theoretical frequency for $L = 10\text{mH}$, $C = 0.01\mu\text{F}$, $0.033\mu\text{F}$ & $0.047\mu\text{F}$

Software Required: - Multisim software, Analog device Edition 13.0

* Components Required *

S.NO	Device	Range	Quantity
1.	DC Supply Voltage	12V	1
	Inductor	5mH	2
	Capacitor	0.22μF	2
		0.01μF	1
		0.033μF	1
	Resistor	0.047μF	1
		1K, 47K, 10K	

2. Oscilloscope 10-20 MHz


3. connecting wires

SA

H


Hartley Oscillator

circuit diagram

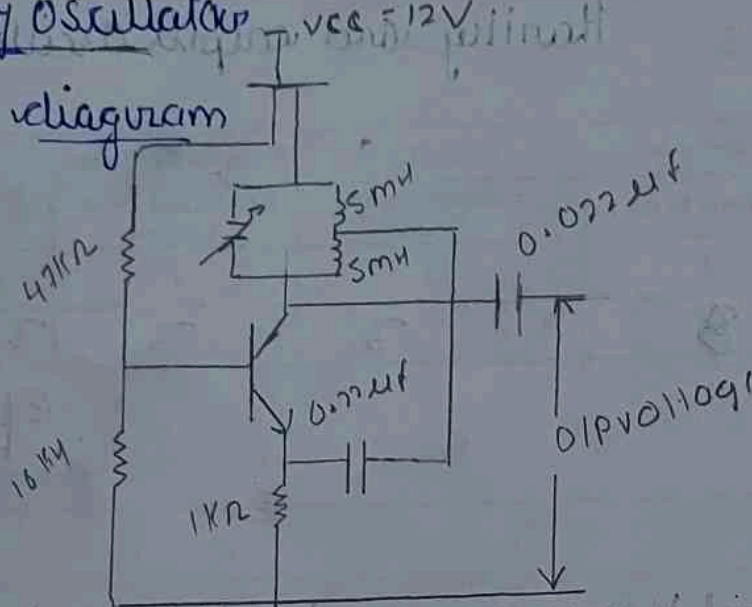


Colpitts Oscillator

circuit diagram

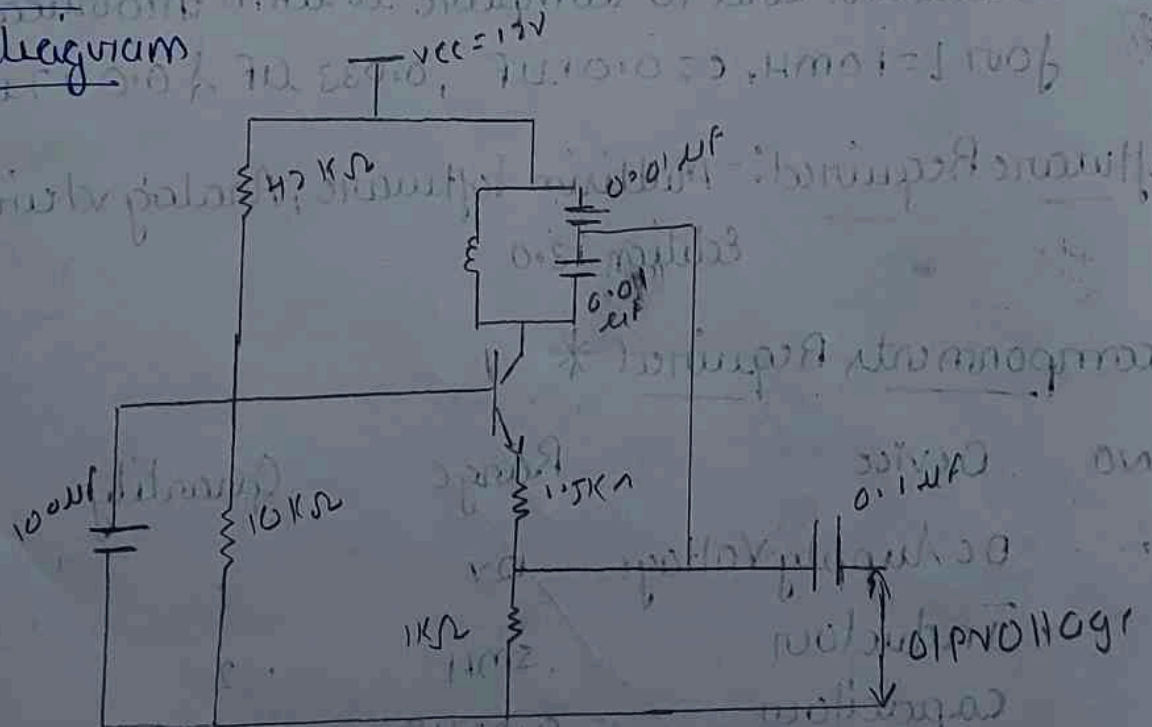

Model waveform

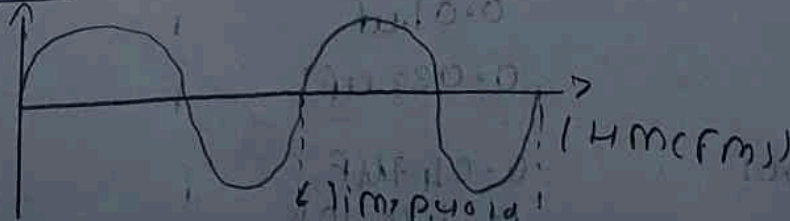

Procedure:- Hartley oscillator

Connect the circuit as shown in figure.

Connect $0.01 \mu F$ capacitor in the circuit and observe the waveform.

Note down the time period of the waveform and calculate the frequency $f = 1/T$

Now connect the capacitance to $0.033 \mu F$ & $0.047 \mu F$ & calculate the frequency and tabulate the reading as shown and the theoretical frequency from the formula $f = \frac{1}{2\pi\sqrt{LC}}$

Where $L_T = L_1 + L_2 = 5mH + 5mH = 10mH$ & compare theoretical & practical values

Capitl Oscillator

Connect the circuit as shown in figure

Connect the $C_2 = 0.001 \mu F$ in the circuit & observe the waveform

Calculate the time period & frequency of the waveform
($f = 1/T$)

Now fix the capacitance to $0.002 \mu F$ then to $0.003 \mu F$ &

Calculate the frequency tabulate the readings as shown

Find theoretical frequency from the Formula $f_0 = \frac{1}{2\pi\sqrt{2\frac{C_1 C_2}{C_1 + C_2}}}$

Compare theoretical & practical values.

Plot the graph o/p voltage vs time period of practical frequency.

Result:- The frequency of oscillation of Hartley & output oscillators is measured practically and compared with theoretical values.

Hardy's Tabular column:-

S.NO.	L (mm)	C (HF)	Throttled Frequency	Time period	Practical Frequency	V ₀ (V)
1.	10	0.01	15.915	64.129 μ s	14.468 kHz	25.604
2.	10	0.033	8.761	120.283 μ s	8.311 kHz	27.162
3.	10	0.047	7.341	142.002 μ s	6.941 kHz	28.251

calculations

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{10 \times 10^{-3} \times 0.01 \times 10^{-6}}} = 15.915 \text{ kHz}$$

$$f = \frac{1}{2\pi\sqrt{10 \times 10^{-3} \times 0.033 \times 10^{-6}}} = 8.761 \text{ kHz}$$

$$f = \frac{1}{2\pi\sqrt{10 \times 10^{-3} \times 0.047 \times 10^{-6}}} = 7.341 \text{ kHz}$$

Kapits Tabular column:-

S.NO.	L (mm)	C ₁ (uF)	C ₂ (uF)	C _T	Throttled Frequency	Practical Frequency	V ₀ (V)
1.	5	0.01	0.001	9.04 $\times 10^{-6}$	74.04 kHz	71.35 kHz	2.422
2.	5	0.01	0.002	1.617 $\times 10^{-5}$	55.17 kHz	50.76 kHz	3.904
3.	5	0.01	0.003	2.307 $\times 10^{-5}$	46.84 kHz	42.51 kHz	5.44

$$C_T = \frac{C_1 C_2}{C_1 + C_2} \quad f = \frac{1}{2\pi\sqrt{LC_T}}$$


$$1. C_T = \frac{0.01 \times 0.001}{0.01 + 0.001} = \frac{10^{-5}}{0.011} = 9.09 \times 10^{-6} \times 10^{-6} = \frac{1}{2\pi\sqrt{5 \times 10^{-3} \times 9.09 \times 10^{-6}}}$$

$$2. f = \frac{1}{2\pi\sqrt{5 \times 10^{-3} \times \left(\frac{0.01 \times 0.002}{0.01 + 0.002} \right) \times 10^{-6}}} = \frac{1}{2\pi\sqrt{5 \times 10^{-3} \times 1.667 \times 10^{-6}}} = 55.127 \text{ kHz}$$

Hardley oscillator at $C = 0.01 \mu F$

Real

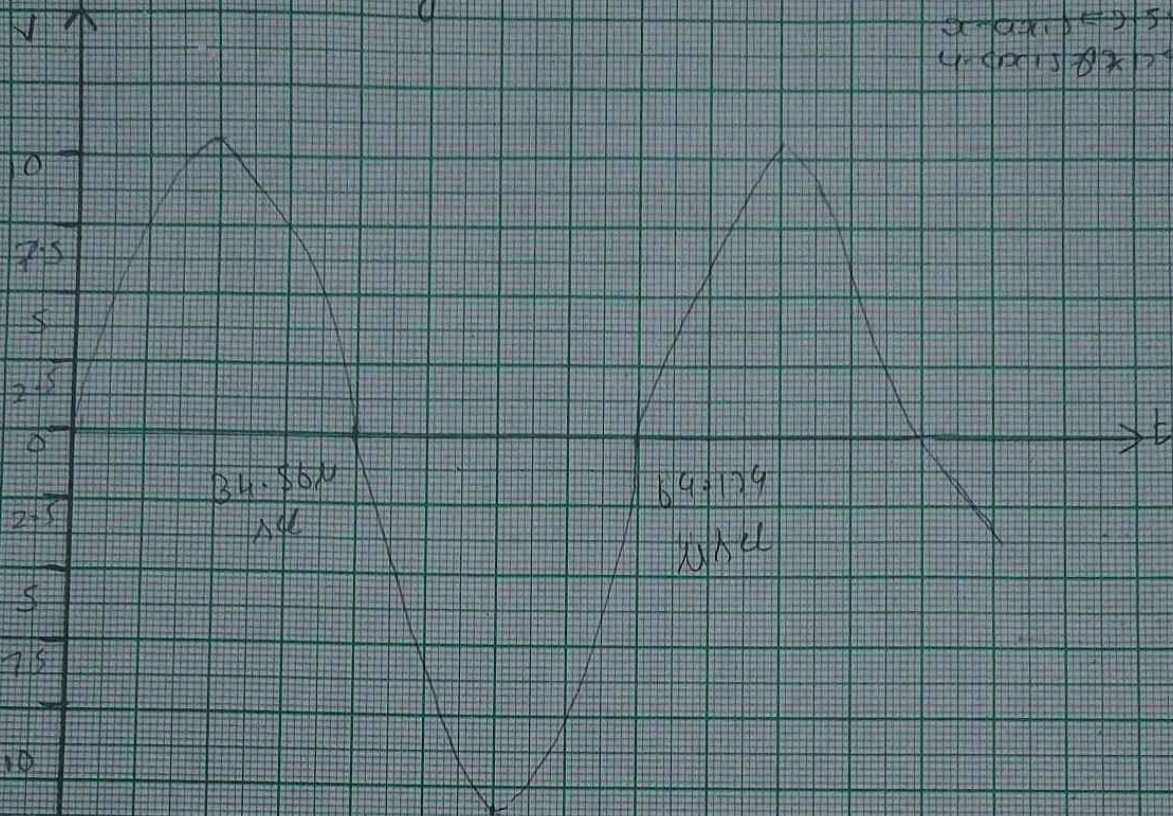$x = 0.15 \text{ V}$
 $y = 0.015 \text{ V}$



Colpitts oscillator at $C_1 = 0.01 \mu F$, $C_2 = 0.001 \mu F$

Real

$x = 0.15 \text{ V}$
 $y = 0.015 \text{ V}$

