



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)
Dundigal, Hyderabad - 500 043

LABORATORY WORK SHEET

Date: 14.06.2021

Roll No: 20951A0494 Name: Mohammed Ahsan

Exp No: 09 Experiment Name: Non linear wave shaping

DAY TO DAY EVALUATION:

	Preparation	Algorithm	Source Code	Program Execution	Viva	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max Marks	4	4	4	4	4	20
Obtained	4	4	4	3	3	18

[Signature]
Signature of Lab VC


START WRITING FROM HERE:

Aim: To study the various clippers and clamper circuits and to plot the output waveforms for a sinusoidal input signal.


Apparatus: -

1. Resistor
2. diode
3. Digital analog discovery kit with PC
4. Dual DC power supply
5. Bread board
6. connecting wires




* Circuit Diagram *

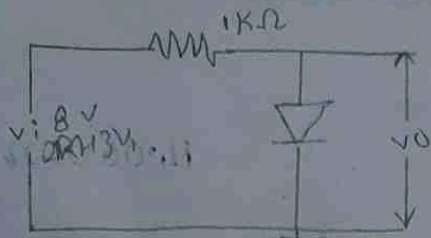






Positive clipping

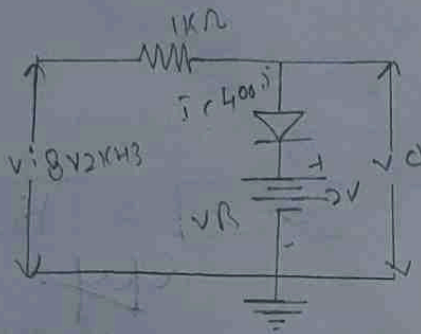






Positive clipping with positive

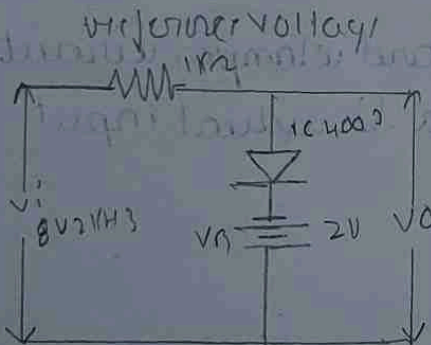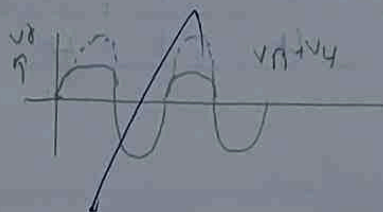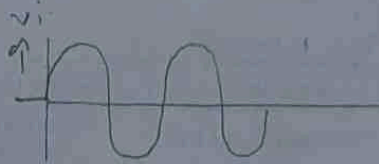

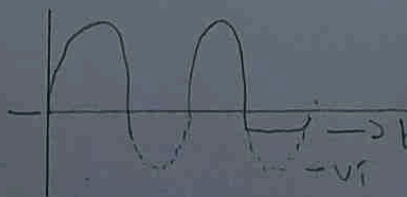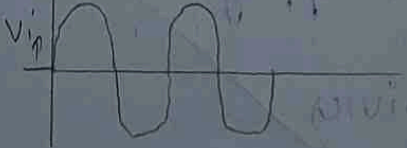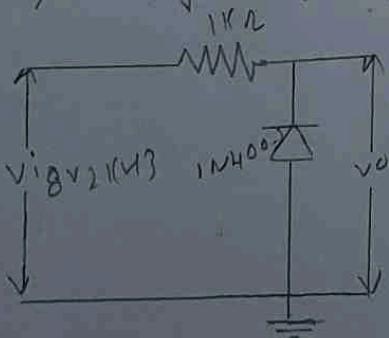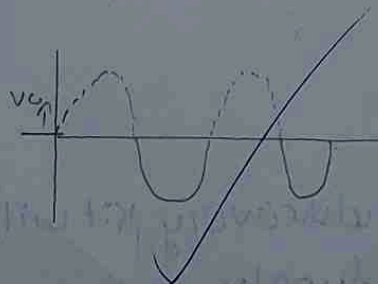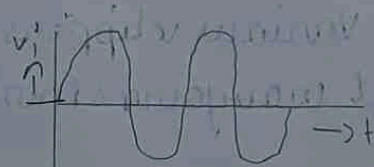Positive clipping with negative Reference Voltage





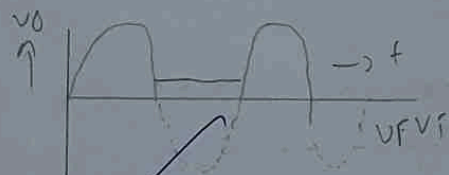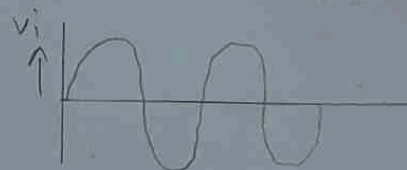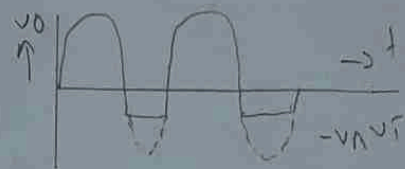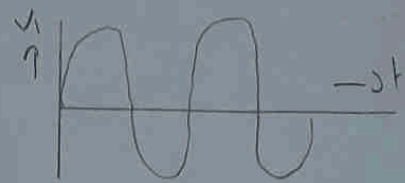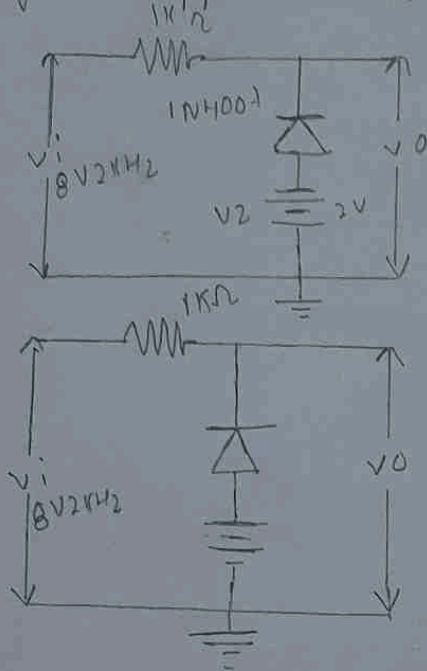Negative clipper with negative Reference voltage





clampers :-



Negative clamper :

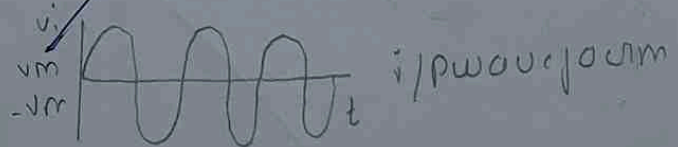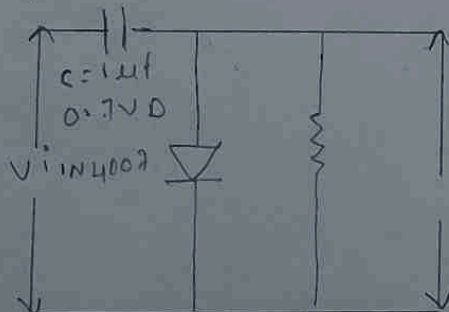

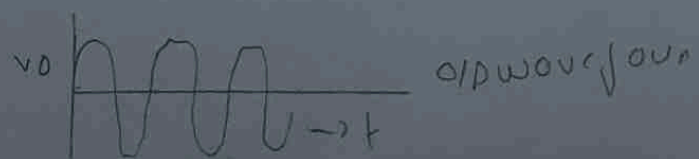
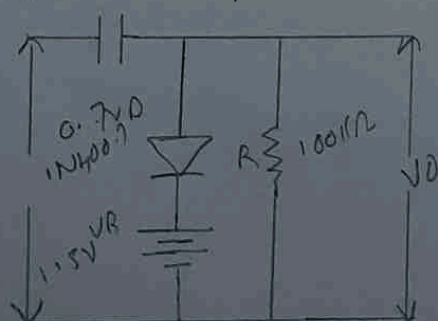
Negative clamping with positive Reference voltage



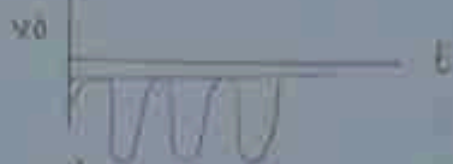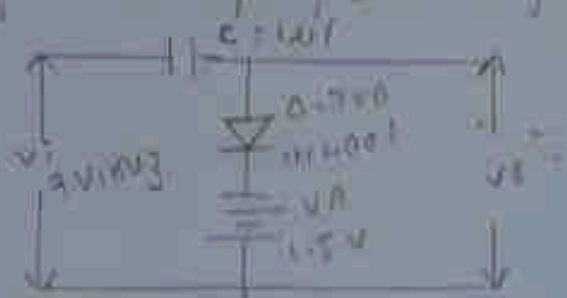
Negative clamping with negative Reference Voltage




Positive clamping

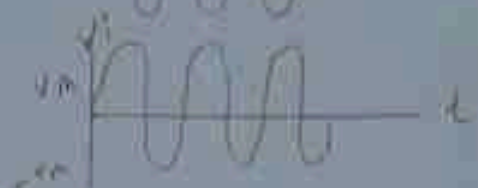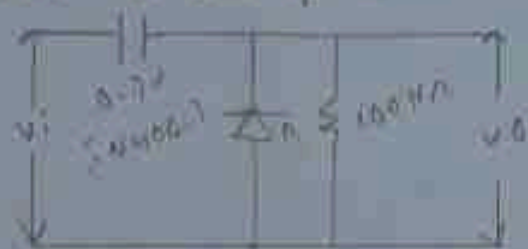

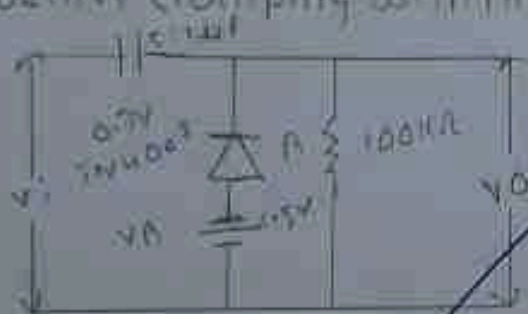Positive clamping with negative Reference Voltage



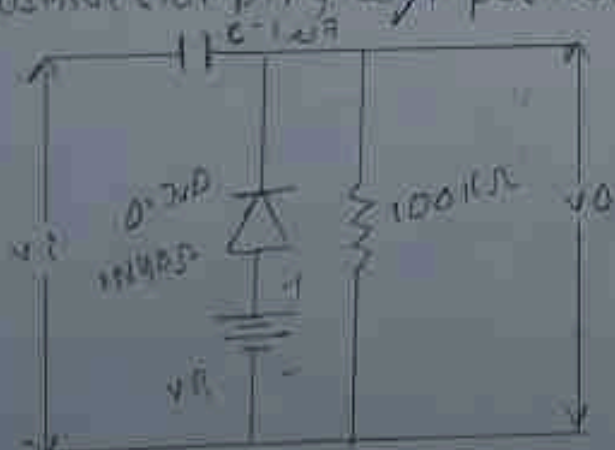Positive clamping with positive reference voltage



* procedure *

- connect the circuit as shown.
- Apply the input sine wave to the circuit ($2V_{pp}$, $2KHz$)
- Switch on the power supply and adjust the output of AF generator to $2V$ (ptop)
- Observe the input & output waveforms on CRO and note down the readings.
- plot the graph of input vs output waveforms for various clipping circuit.

* Tabular column *


Type of clipper	Reference volts	
Positive clipper	0V	$V_{max} = 24mV$, $V_{min} = 44.8mV$
	2V	$V_{max} = 0.5V$, $V_{min} = 2.03V$
	-2V	$V_{max} = 2.5V$, $V_{min} = 2.03V$
Negative clipper	0V	$V_{max} = 24mV$, $V_{min} = 44.8mV$
	2V	$V_{max} = 2.03V$, $V_{min} = 2.0V$
	-2V	$V_{max} = 0.5V$, $V_{min} = 2.0V$

Type of clamper	Reference volt	
positive clamper	1/p = 10V	$V_{max} = 0V$, $V_{min} = 2.25V$
negative clamper	1/p = 10V	$V_{max} = 44.8V$, $V_{min} = 0$


* Result *

Hence plotted the output waveform of various clipper & clamper for sinusoidal input.


CS

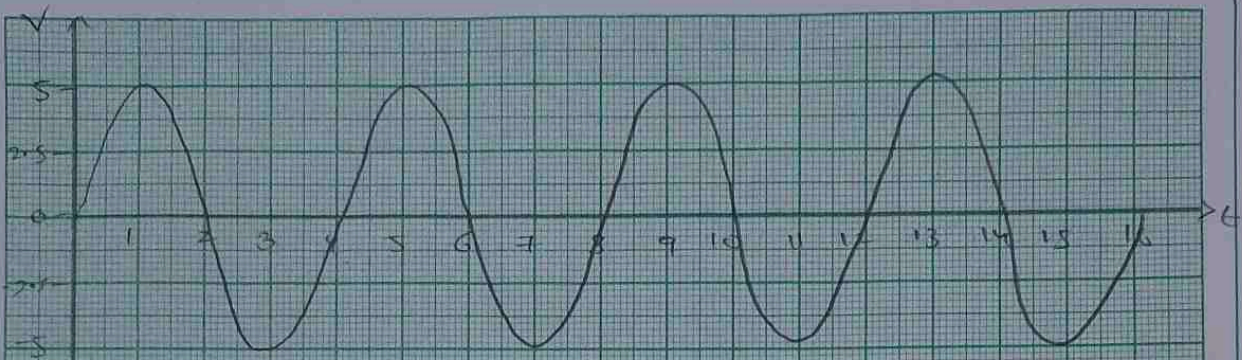


Positive Clipper

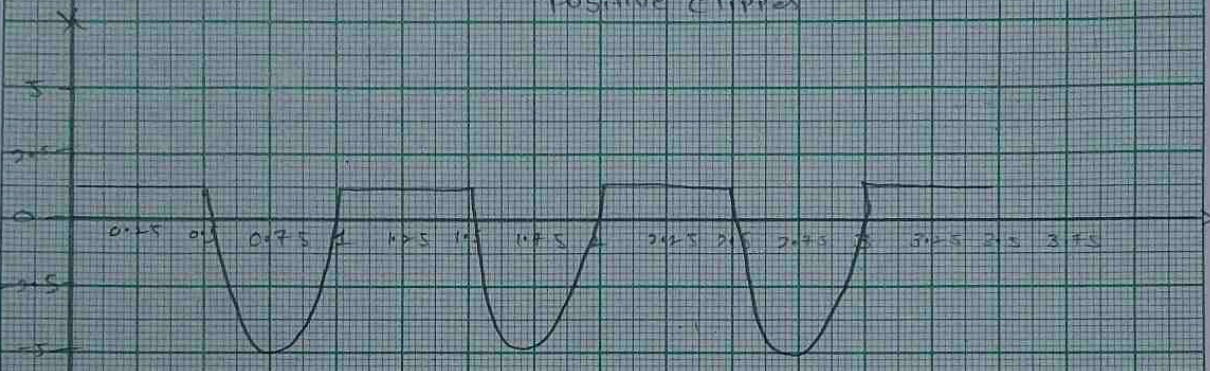


Positive clipper with reference

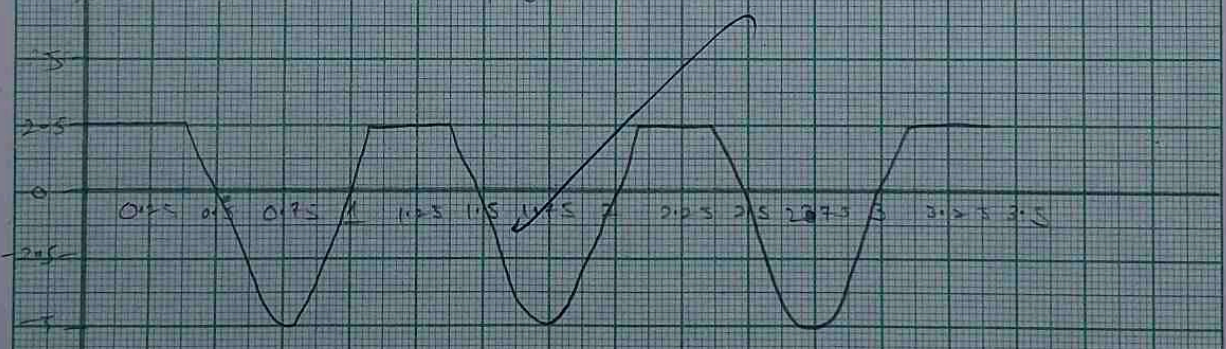


Negative clipper

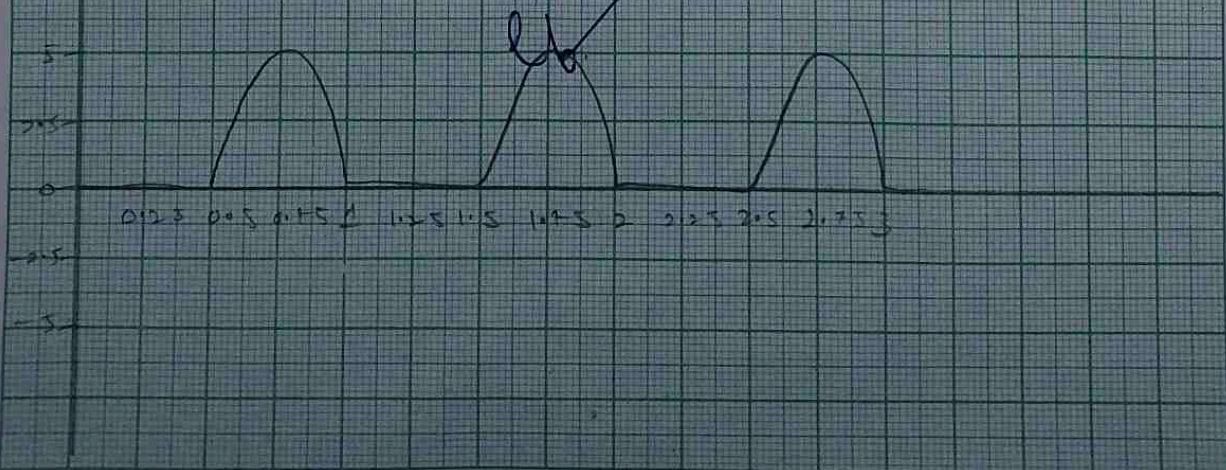


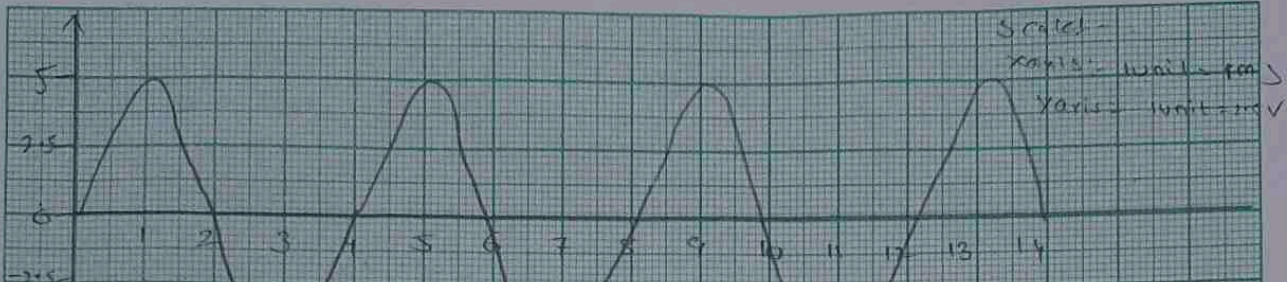


positive clamper

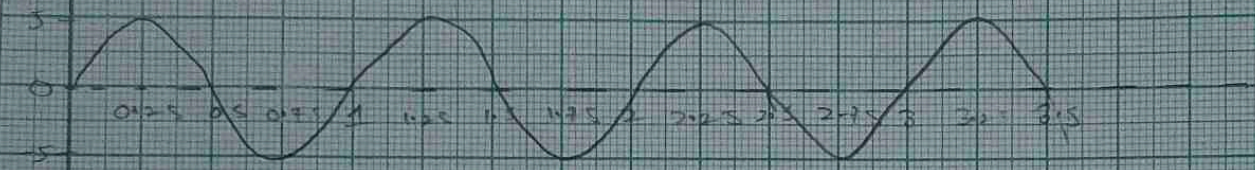

positive clamper with reference

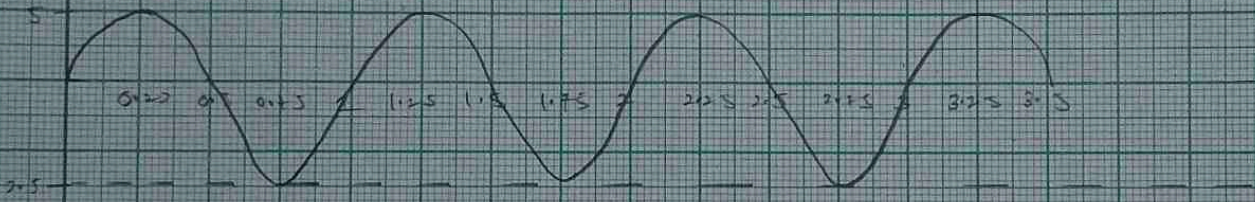

Negative

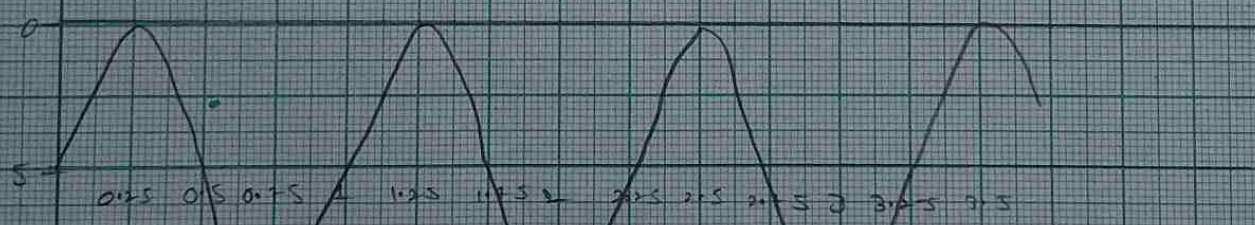

Negative clamper with reference

